

CDA 3200 Digital Systems

Instructor: Dr. Janusz Zalewski

Developed by: Dr. Dahai Guo

Spring 2012

Outline

- Overview of VHDL
- VHDL Description of Combinational Circuits
- VHDL Models for Multiplexers
- VHDL Modules
- Signals and Constants
- Arrays
- VHDL Operators
- Packages and Libraries

Overview of VHDL (1/6)

- VHDL
 - VHSIC Hardware Description Language
 - VHSIC: Very High Speed Integrated Circuit
 - Widely used in the industry

Overview of VHDL (2/6)

- Why VHDL?
 - Detailed design of the systems at the gate level has become very tedious and time consuming.
 - A hardware description language of top-down methodology is desired.

Overview of VHDL (3/6)


- The program that designs a 3-bit adder
 1. entity ADD is
 2. port (A, B : in integer range 0 to 7;
 3. Z : out integer range 0 to 15);
 4. end ADD;

 5. architecture ARITHMETIC of ADD is
 6. begin
 7. Z <= A + B;
 8. end ARITHMETIC;

Overview of VHDL (4/6)

- It seems that Boolean algebra, Karnaugh-Maps, and other techniques (Quine-McCluskey and Petrick's methods) are useless, if VHDL is so powerful.

Overview of VHDL (5/6)

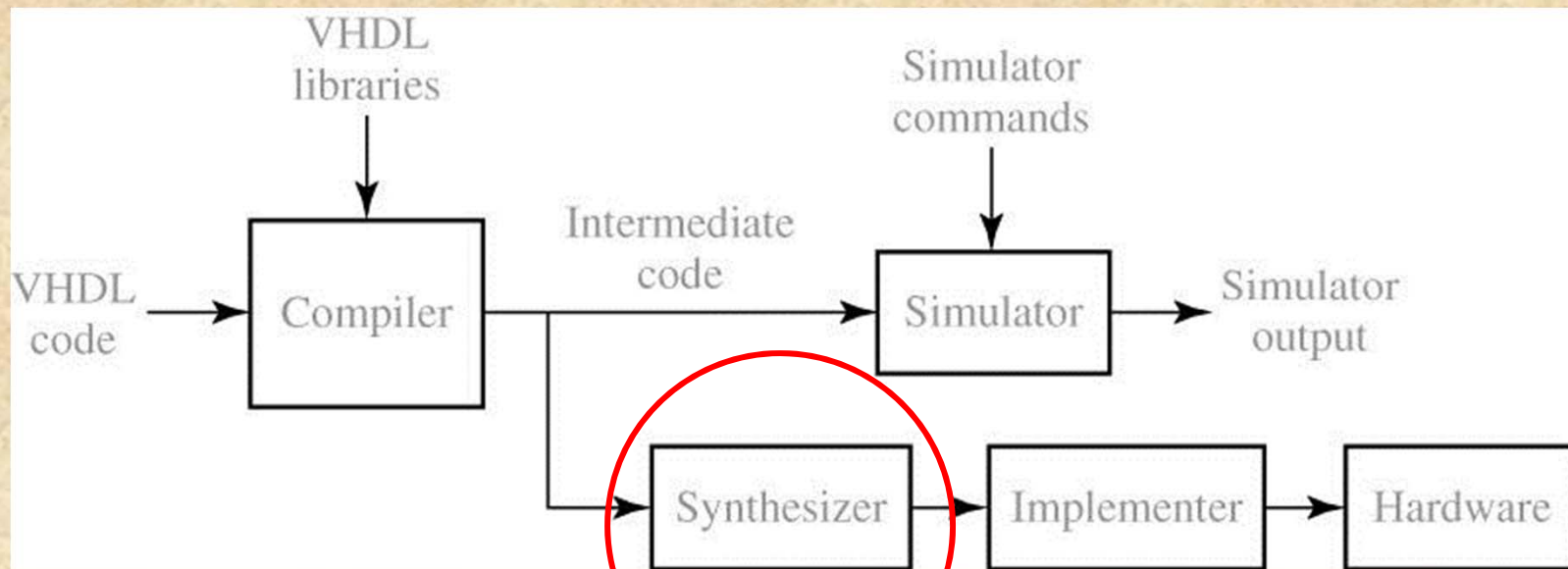


Where Boolean algebra, Karnaugh maps and other methods are integrated.

Overview of VHDL (6/6)

- Because the simplifying methods are systematic, they can be programmed into the synthesizer.
- Therefore, hardware designers can be freed of detailed work at the gate level.
- But the designers still can work at the gate level in VHDL.

VHDL Description of Combinational Circuits (1/6)

 - Signal assignment operator
 1. $C \leftarrow A \text{ and } B$ *after* 5 ns;
 2. $E \leftarrow C \text{ or } D$ *after* 5 ns;



- Logically equivalent?
 1. $E \leftarrow C \text{ or } D$ *after* 5 ns;
 2. $C \leftarrow A \text{ and } B$ *after* 5 ns;

VHDL Description of Combinational Circuits (2/6)


- VHDL signal assignment statements are concurrent statements.
 - The VHDL simulator monitors the right side of each concurrent statement;
 - Any time a signal changes, the expression on the right side is immediately re-evaluated;
 - The new value is assigned to the signal on the left side after the delay.
 - The order of the concurrent statements does not matter.

VHDL Description of Combinational Circuits (3/6)

- The delay is optional in assignment statements.
 - $E \leq C \text{ or } D;$
 - $C \leq A \text{ and } B;$
 - When no delay is specified, the simulator will assume an infinitesimal delay referred to as Δ (delta).

VHDL Description of Combinational Circuits (4/6)

- Clock
 - CLK <= not CLK after 10 ns;

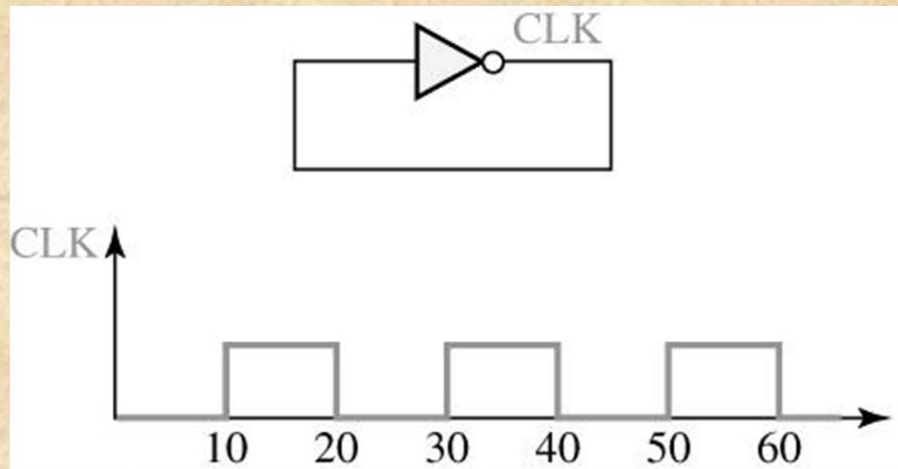

No, because a run-time error during simulation will be caused.

Can we remove the delay?

VHDL Description of Combinational Circuits (5/6)

- Bit vectors

- B <= "0110";

- A <= "1100";


- C <= A and B; **↔** C(3) <= A(3) and B(3);
C(2) <= A(2) and B(2);
C(1) <= A(1) and B(1);
C(0) <= A(0) and B(0);

VHDL Description of Combinational Circuits (6/6)

- Comments are preceded by --
- An identifier, such as a variable, must start with a letter, and it cannot end with an underscore.
- Each statement is ended with a semicolon.
- NOT CASE SENSITIVE


VHDL Models for Multiplexers (1/6)

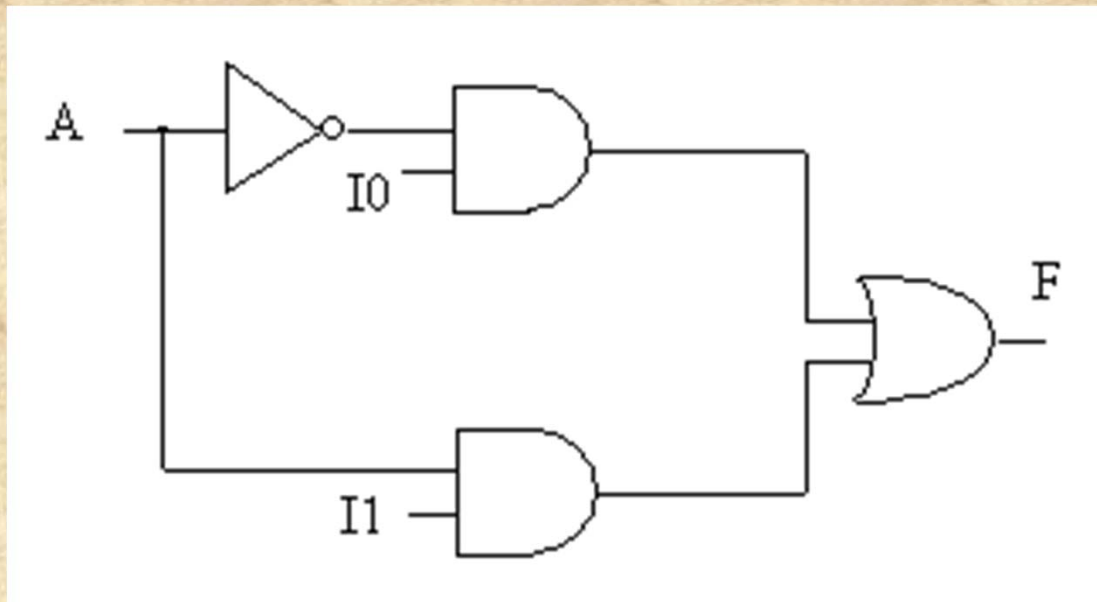- 2-to-1 multiplexer
 - $F \leq (\text{not } A \text{ and } I0) \text{ or } (A \text{ and } I1);$




VHDL Models for Multiplexers (2/6)

 
- 2-to-1 (cont)
 1. -- conditional signal assignment statement
 2. $F \leq I0$ when $A='0'$ else $I1$;



VHDL Models for Multiplexers (3/6)

 

Design at the gate level.

 


Design at the logic level.

VHDL Models for Multiplexers (4/6)

- The general form of a conditional signal assignment statement is
 1. `signal_name <= expression1 when condition1`
 2. `else expression2 when condition2`
 3. `.....`
 4. `[else expressionN];`
 - This concurrent statement is executed whenever a change occurs in a signal used in the selected expression or its condition.

VHDL Models for Multiplexers (5/6)


- 4-to-1

 

```
F <= I0 when A&B="00"  
     I1 when A&B="01"  
     I2 when A&B="10"  
     I3;
```

VHDL Models for Multiplexers (6/6)

- 4-to-1

 

```
sel <= A&B;  
with sel select  
  F <= I0 when "00",  
      I1 when "01",  
      I2 when "10",  
      I3 when "11";
```

VHDL Modules (1/17)

- Entities and architectures
 - An entity declares the interface between a module and its environment. What are the input(s) and output(s)?
 - The architecture contains the implementation for an entity.

VHDL Modules (2/17)

- An entity does not deal with design details.

- Example:

- entity two_gates is

- port (A, B, D: in bit; E: out bit);

- end two_gates;

- Key words that are used to define an entity.
- The name of the entity.
- The input and output list. **port** is a key word that is used to declare input/output
- A, B, D are the input signals and E is the output signal.
- Be careful where you need semicolons, commas, and colons.

VHDL Modules (3/17)

- Associated with each entity is one or more architecture declarations

- architecture gates of two_gates is

- signal C: bit;

- begin

- C <= A and B; -- concurrent

- E <= C or D; -- statements

- end gates;

- Key words used to define an architecture.

- Every architecture must be associated with an entity.

- The architecture's name.

- Signal used within this architecture.

- Design details

VHDL Modules (4/17)

- Full adder
 - entity FullAdder is
 - port(X, Y, Cin: in bit; -- inputs
 - Cout, Sum: out bit); -- outputs
 - end FullAdder;

VHDL Modules (5/17)


- Full adder

- architecture Equations of *FullAdder* is
- begin
- Sum <= X xor Y xor Cin after 10 ns;
- Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
- end Equations;

VHDL does not specify an order of precedence for the logic operators, therefore parentheses are required.

VHDL Modules (6/17)

- 4-bit full adder

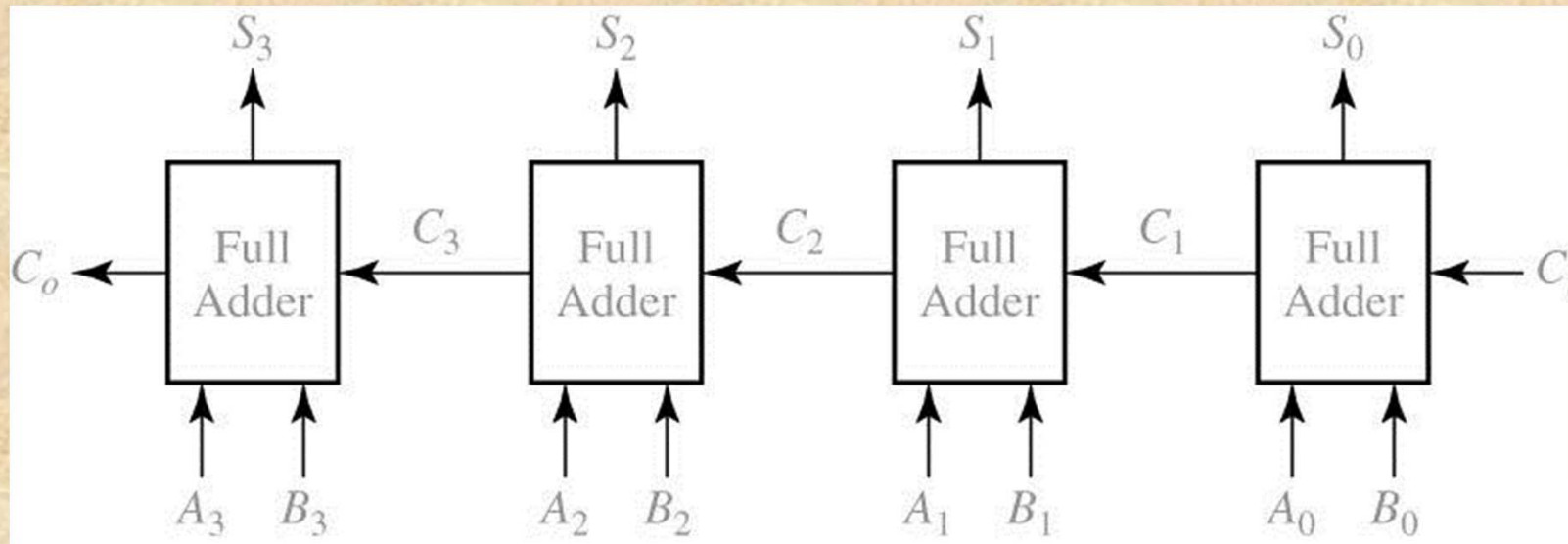

1. entity Adder4 is
2. port (A, B: in bit_vector(3 downto 0); Ci: in bit -- Inputs
3. S: out bit_vector(3 downto 0); Co: out bit) -- Outputs
4. Adder4
5. architecture Structure of adder4 is
6. begin

1. $S(0) \leq A(0) \text{ xor } B(0) \text{ xor } Ci(0)$ after 10 ns;
2. $Co(0) \leq (A(0) \text{ and } B(0)) \text{ or } (A(0) \text{ and } Ci(0)) \text{ or } (B(0) \text{ and } Ci(0))$ after 10 ns;

Find all the syntax errors in lines 1-6 and 15.

3. $S(1) \leq A(1) \text{ xor } B(1) \text{ xor } Ci(1)$ after 10 ns;
4. $Co(1) \leq (A(1) \text{ and } B(1)) \text{ or } (A(1) \text{ and } Ci(1)) \text{ or } (B(1) \text{ and } Ci(1))$ after 10 ns;
5. $S(2) \leq A(2) \text{ xor } B(2) \text{ xor } Ci(2)$ after 10 ns;
6. $Co(2) \leq (A(2) \text{ and } B(2)) \text{ or } (A(2) \text{ and } Ci(2)) \text{ or } (B(2) \text{ and } Ci(2))$ after 10 ns;
7. $S(3) \leq A(3) \text{ xor } B(3) \text{ xor } Ci(3)$ after 10 ns;
8. $Co(3) \leq (A(3) \text{ and } B(3)) \text{ or } (A(3) \text{ and } Ci(3)) \text{ or } (B(3) \text{ and } Ci(3))$ after 10 ns;

9. Structure

1. entity Adder4 is
2. port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
3. S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
4. **end** Adder4;
5. architecture Structure of adder4 is
6. begin

7. S(0) <= A(0) xor B(0) xor Ci(0) after 10 ns;
8. Co(0) <= (A(0) and B(0)) or (A(0) and Ci(0)) or (B(0) and Ci(0)) after 10 ns;
- Find all the syntax errors in lines 1-6 and 15.***
9. S(1) <= A(1) xor B(1) xor Ci(1) after 10 ns;
10. Co(1) <= (A(1) and B(1)) or (A(1) and Ci(1)) or (B(1) and Ci(1)) after 10 ns;

11. S(2) <= A(2) xor B(2) xor Ci(2) after 10 ns;
12. Co(2) <= (A(2) and B(2)) or (A(2) and Ci(2)) or (B(2) and Ci(2)) after 10 ns;

13. S(3) <= A(3) xor B(3) xor Ci(3) after 10 ns;
14. Co(3) <= (A(3) and B(3)) or (A(3) and Ci(3)) or (B(3) and Ci(3)) after 10 ns;

- 15.**end** Structure;

1. entity Adder4 is
2. port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
3. S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
4. end Adder4;
5. architecture Structure of adder4 is
6. begin

In this paragraph?

7. S(0) <= A(0) xor B(0) xor Ci(0) after 10 ns;
8. Co(0) <= (A(0) and B(0)) or (A(0) and Ci(0)) or (B(0) and Ci(0)) after 10 ns;

9. S(1) <= A(1) xor B(1) xor Ci(1) after 10 ns;
10. Co(1) <= (A(1) and B(1)) or (A(1) and Ci(1)) or (B(1) and Ci(1)) after 10 ns;

11. S(2) <= A(2) xor B(2) xor Ci(2) after 10 ns;
12. Co(2) <= (A(2) and B(2)) or (A(2) and Ci(2)) or (B(2) and Ci(2)) after 10 ns;

13. S(3) <= A(3) xor B(3) xor Ci(3) after 10 ns;
14. Co(3) <= (A(3) and B(3)) or (A(3) and Ci(3)) or (B(3) and Ci(3)) after 10 ns;

15. end Structure;

VHDL Modules (10/17)

- 4-bit full adder
 1. $S(0) \leq A(0) \text{ xor } B(0) \text{ xor } \underline{Ci(0)}$ after 10 ns;
 2. $Co(0) \leq (A(0) \text{ and } B(0)) \text{ or } (A(0) \text{ and } Ci(0)) \text{ or } (B(0) \text{ and } Ci(0))$ after 10 ns;
 - Ci and Co are defined as bit signals and cannot work with indices.

VHDL Modules (11/17)

- 4-bit full adder
 - architecture Structure of Adder4 is
 - signal C:bit vector(2 downto 0);
 - begin
 - end Structure;

VHDL Modules (12/17)

- $S(0) \leq A(0) \text{ xor } B(0) \text{ xor } C_i$ after 10 ns;
- $C(0) \leq (A(0) \text{ and } B(0)) \text{ or } (A(0) \text{ and } C_i) \text{ or } (B(0) \text{ and } C_i)$ after 10 ns;
- $S(1) \leq A(1) \text{ xor } B(1) \text{ xor } C(0)$ after 10 ns;
- $C(1) \leq (A(1) \text{ and } B(1)) \text{ or } (A(1) \text{ and } C(0)) \text{ or } (B(1) \text{ and } C(0))$ after 10 ns;
- $S(2) \leq A(2) \text{ xor } B(2) \text{ xor } C(1)$ after 10 ns;
- $C(2) \leq (A(2) \text{ and } B(2)) \text{ or } (A(2) \text{ and } C(1)) \text{ or } (B(2) \text{ and } C(1))$ after 10 ns;
- $S(3) \leq A(3) \text{ xor } B(3) \text{ xor } C(2)$ after 10 ns;
- $C_o \leq (A(3) \text{ and } B(3)) \text{ or } (A(3) \text{ and } C(2)) \text{ or } (B(3) \text{ and } C(2))$ after 10 ns;

VHDL Modules (13/17)

- 4-bit full adder
 - Simulation commands
 - *list A B Co C Ci S* -- put these signals on the output list
 - *force A 1111* -- set the A inputs to 1111
 - *force B 0001* -- set the B inputs to 0001
 - *force Ci 1* -- set Ci to 1
 - *run 50 ns* -- run the simulation for 50 ns

VHDL Modules (14/17)

- 4-bit full adder
 - Simulation output

| | Current | 0ns | 10ns | 20ns | 30ns | 40ns | 50ns | |
|----|---------|-----|------|------|------|------|------|--|
| A | 1111 | F | | | | | | |
| B | 0001 | 1 | | | | | | |
| Ci | '1' | | | | | | | |
| S | 0001 | 0 | F | D | 9 | 1 | | |
| Co | '1' | | | | | | 1 | |
| C | 111 | 0 | 1 | 3 | 7 | | | |

VHDL Modules (15/17)

- Since a 4-bit full adder is a sequence of 1-bit full adders, why do not we build the 4-bit adder based on 1-bit adders in VHDL?
 - -- specify the FullAdder as a component
 - -- within the architecture of Adder4
 - architecture Structure of *Adder4* is
 - ***component FullAdder***
 - port (X, Y, Cin: in bit; -- Inputs
 - Cout, Sum: out bit); -- Outputs
 - ***end component;***
 - -- *other code*
 - end Structure;


VHDL Modules (16/17)

- *-- other code*
- *signal C: bit_vector(3 downto 1);*
- *begin --instantiate four copies of the FullAdder*
- *FA0: FullAdder port map (A(0), B(0), Ci, C(0), S(0));*
- *FA1: FullAdder port map (A(1), B(1), C(0), C(1), S(1));*
- *FA2: FullAdder port map (A(2), B(2), C(1), C(2), S(2));*
- *FA3: FullAdder port map (A(3), B(3), C(2), Co, S(3));*


VHDL Modules (17/17)


- Component instantiation statements
 - label: component-name ***port map*** (list-of-actual-signals)

4-bit Full Adder Simulation (1/7)

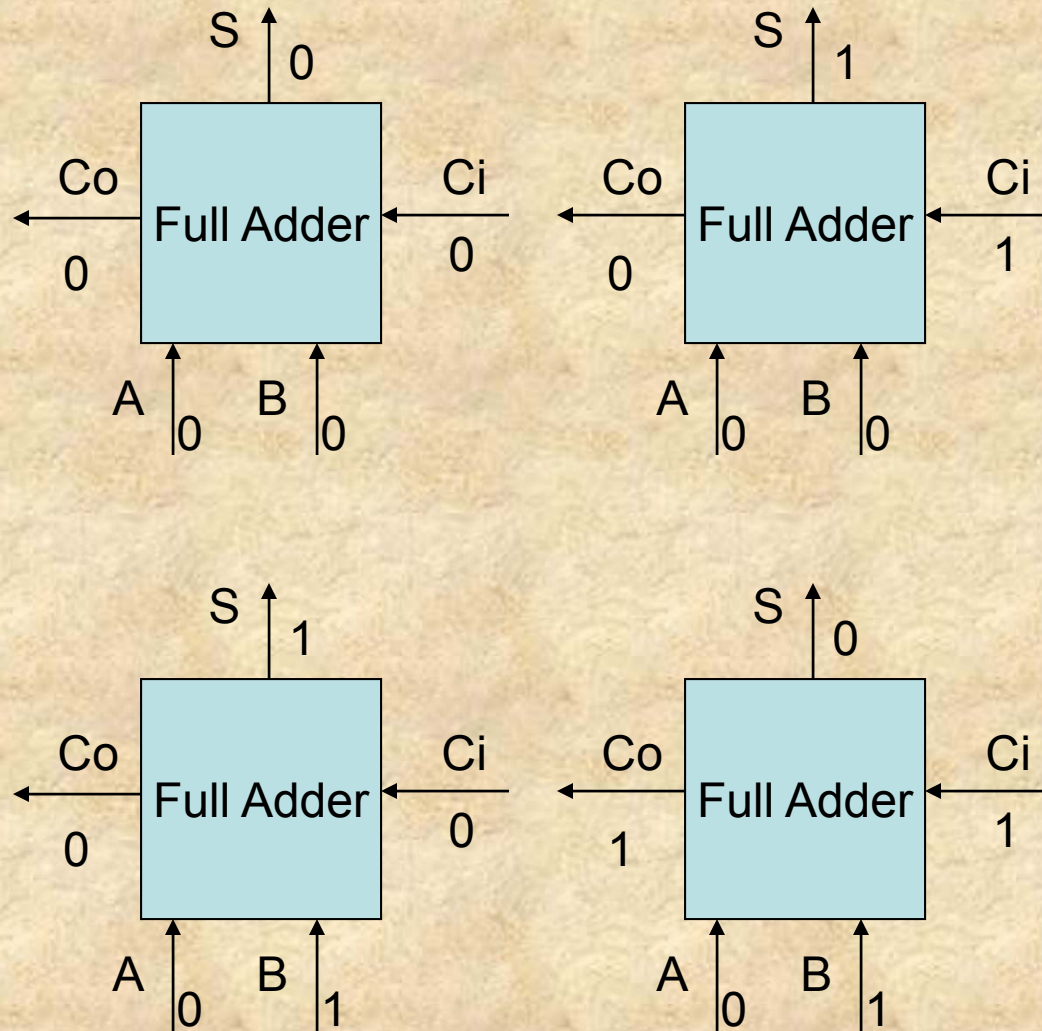

4-bit Full Adder Simulation (2/7)

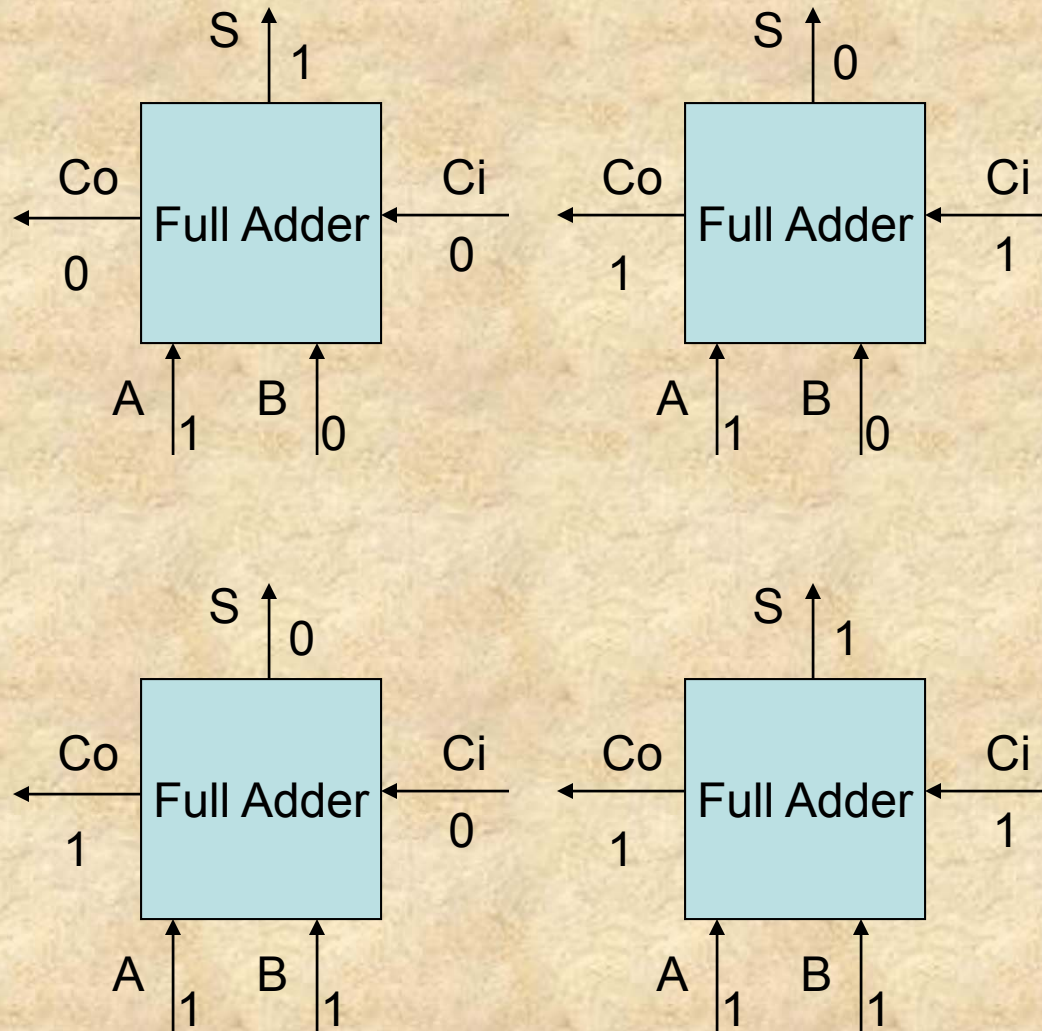


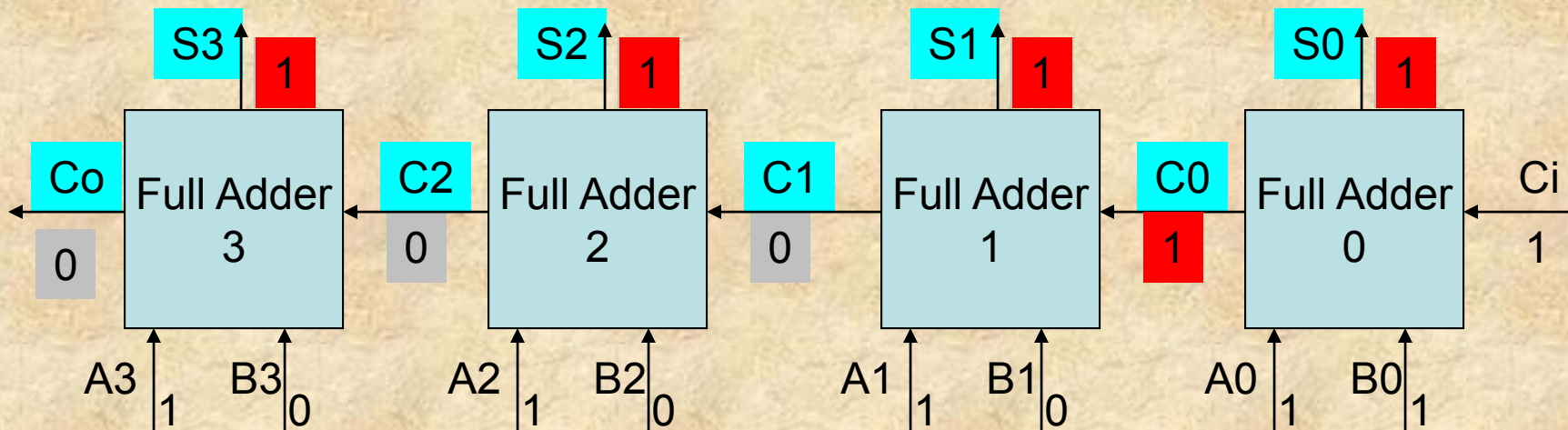

| | C2 | C1 | C0 | S3 | S2 | S1 | S0 | Co |
|------|----|----|------|----|----|----|------|----|
| 0ns | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10ns | 0 | 0 | 1(1) | 1 | 1 | 1 | 1(F) | 0 |

| | Current | 0ns | 10ns | 20ns | 30ns | 40ns | 50ns |
|----|---------|-----|------|------|------|------|------|
| A | 1111 | F | | | | | |
| B | 0001 | 1 | | | | | |
| Ci | '1' | | | | | | |
| S | 1111 | 0 | | | | | |
| Co | '0' | F | | | | | |
| C | 001 | 0 | | | | | |

4-bit Full Adder Simulation (3/8)

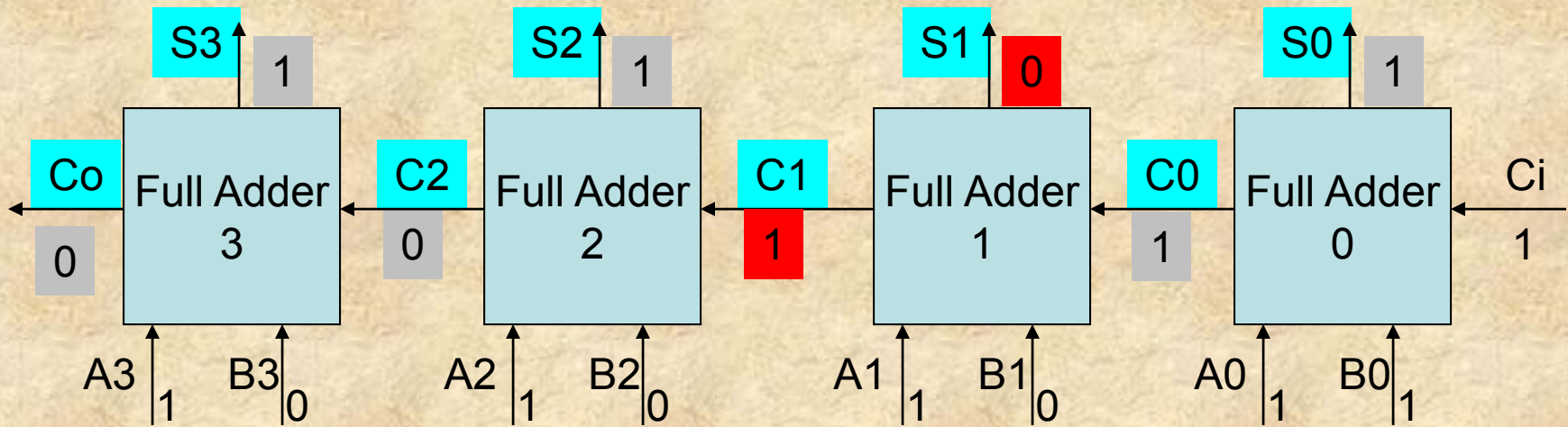


| | C2 | C1 | C0 | S3 | S2 | S1 | S0 | Co |
|------|----|----|------|----|----|----|------|----|
| 0ns | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10ns | 0 | 0 | 1(1) | 1 | 1 | 1 | 1(F) | 0 |
| 20ns | 0 | 1 | 1(3) | 1 | 1 | 0 | 1(D) | 0 |

Nothing changes to the inputs of Full Adders 0,2,3. Only need to look at Full Adder 1.


| | Current | 0ns | 10ns | 20ns | 30ns | 40ns | 50ns |
|----|---------|-----|------|------|------|------|------|
| A | 1111 | F | | | | | |
| B | 0001 | 1 | | | | | |
| Ci | '1' | | | | | | |
| S | 1101 | 0 | F | D | | | |
| Co | '0' | | | | | | |
| C | 011 | 0 | 1 | 3 | | | |

4-bit Full Adder Simulation (4/8)

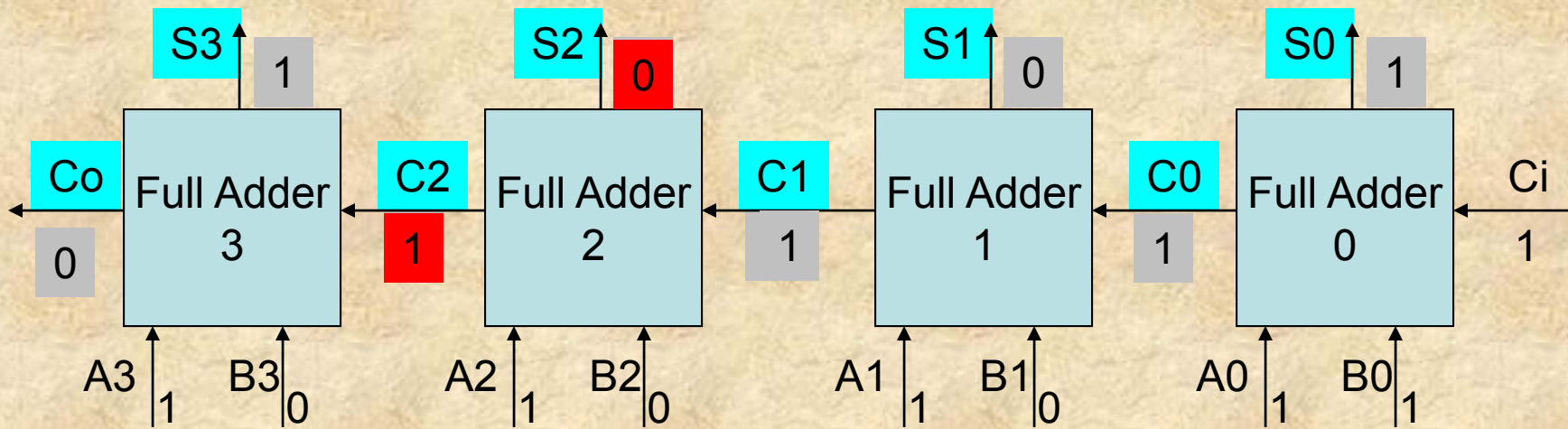


| | C2 | C1 | C0 | S3 | S2 | S1 | S0 | Co |
|------|----|----|------|----|----|----|------|----|
| 0ns | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10ns | 0 | 0 | 1(1) | 1 | 1 | 1 | 1(F) | 0 |
| 20ns | 0 | 1 | 1(3) | 1 | 1 | 0 | 1(D) | 0 |
| 30ns | 1 | 1 | 1(7) | 1 | 0 | 0 | 1(9) | 0 |

 Nothing changes to the inputs of Full Adders 0,1,3. Only need to look at Full Adder 2.




4-bit Full Adder Simulation (5/8)

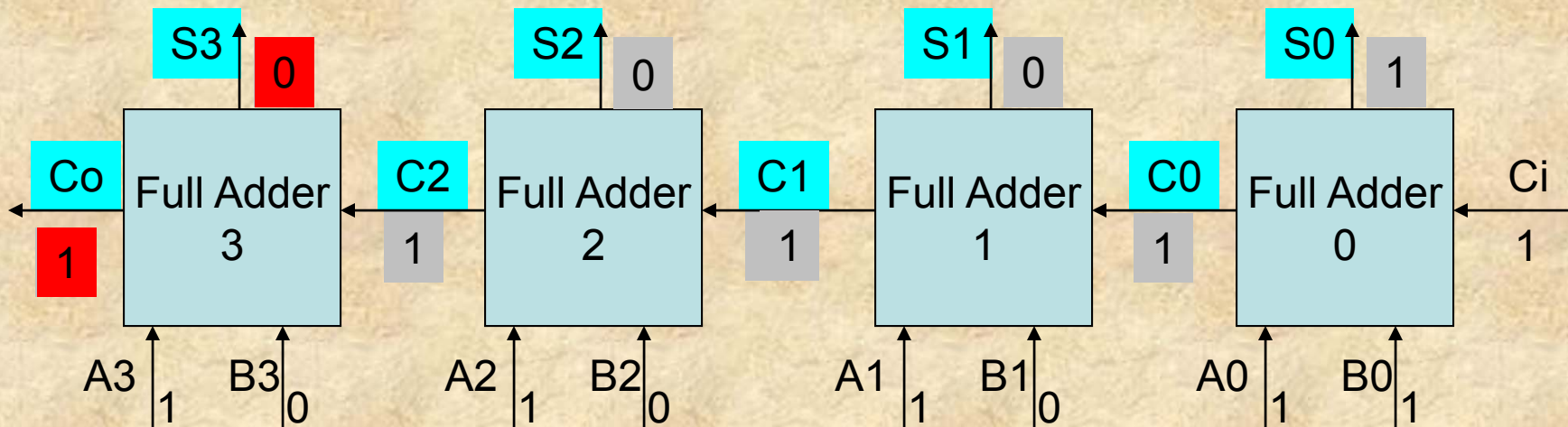


| | C2 | C1 | C0 | S3 | S2 | S1 | S0 | Co |
|------|----|----|------|----|----|----|------|----|
| 0ns | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10ns | 0 | 0 | 1(1) | 1 | 1 | 1 | 1(F) | 0 |
| 20ns | 0 | 1 | 1(3) | 1 | 1 | 0 | 1(D) | 0 |
| 30ns | 1 | 1 | 1(7) | 1 | 0 | 0 | 1(9) | 0 |
| 40ns | 1 | 1 | 1(7) | 0 | 0 | 0 | 1(1) | 1 |

 Nothing changes to the inputs of Full Adders 0,1,2. Only need to look at Full Adder 3




4-bit Full Adder Simulation (6/8)

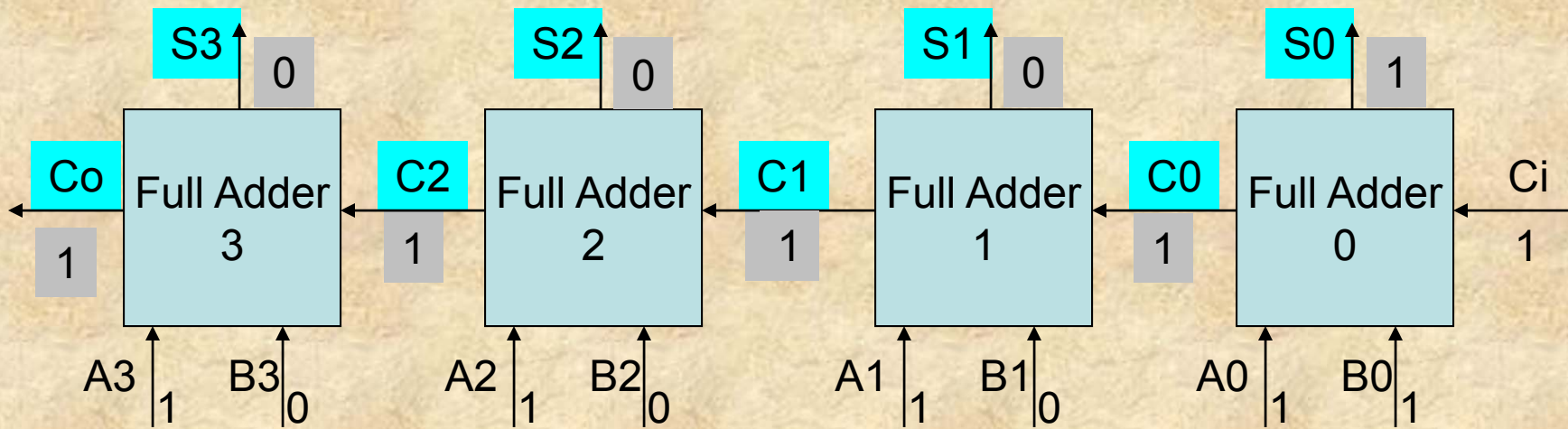

| | C2 | C1 | C0 | S3 | S2 | S1 | S0 | Co |
|------|----|----|------|----|----|----|------|----|
| 0ns | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10ns | 0 | 0 | 1(1) | 1 | 1 | 1 | 1(F) | 0 |
| 20ns | 0 | 1 | 1(3) | 1 | 1 | 0 | 1(D) | 0 |
| 30ns | 1 | 1 | 1(7) | 1 | 0 | 0 | 1(9) | 0 |
| 40ns | 1 | 1 | 1(7) | 0 | 0 | 0 | 1(1) | 1 |
| 50ns | 1 | 1 | 1(7) | 0 | 0 | 0 | 1(1) | 1 |

 The circuit is steady.
Nothing changes
from 40-50 ns.



4-bit Full Adder
Simulation (7/8)

Signals and Constants (1/5)

- Signals
 - Interface: input/output
 - entity FullAdder is
 - port(X, Y, Cin: in bit; -- inputs
 - Cout, Sum: out bit); -- outputs
 - end FullAdder;
 - Internal signals
 - architecture gates of two_gates is
 - signal C: bit;
 - begin
 - C <= A and B; -- concurrent
 - E <= C or D; -- statements
 - end gates;

Signals and Constants (2/5)

- The predefined VHDL types
 - bit: '0' or '1'
 - boolean: FALSE or TRUE
 - integer
 - positive
 - natural
 - real
 - character
 - time

Signals and Constants (2/5) (cont)

| | |
|-------------|---------------|
| – Types | default value |
| – bit | '0' |
| – Boolean | false |
| – integer | not defined |
| – positive | 1 |
| – natural | 0 |
| – Real | 0.000 |
| – character | not defined |
| – Time | 0 |

Signals and Constants (3/5)

- Signal initialization
 - signal A: bit := '1'; -- A <= '1'
 - signal A:bit; -- A<='0'. '0' is the default value
 - signal A,B,C:bit = '1'; -- anything wrong?
 - signal A,B,C:bit := '1'; -- what are A and B?
 - -- all A, B, and C will be
 - -- initialized to '1'

Signals and Constants (4/5)

- Constants:
 - **constant** limit:integer := 17;
 - **constant** delay1:time := 5 ns;
 - A <= B after delay1;

Signals and Constants (5/5)

- Enumeration data type
 - Defined by users
 - **type** state_type **is** (S0,S1,S2,S3,S4,S5);
 - signal state : state_type := S1;
 - state <= s3;

Arrays (1/11)

- Differences with arrays in Java/C++
 - Index values can be customized.
 - Must create an array type before declaring an array object.


Arrays (2/11)

- Differences with arrays in Java/C++ (cont)
 - Correct declaration
 - type SHORT_WORD is array (15 downto 0) of bit;
 - signal DATA_WORD : SHORT_WORD;
 - Wrong declaration
 - signal DATA_WORD : array (15 downto 0) of bit;

Arrays (3/11)

- Differences with arrays in Java/C++ (cont)

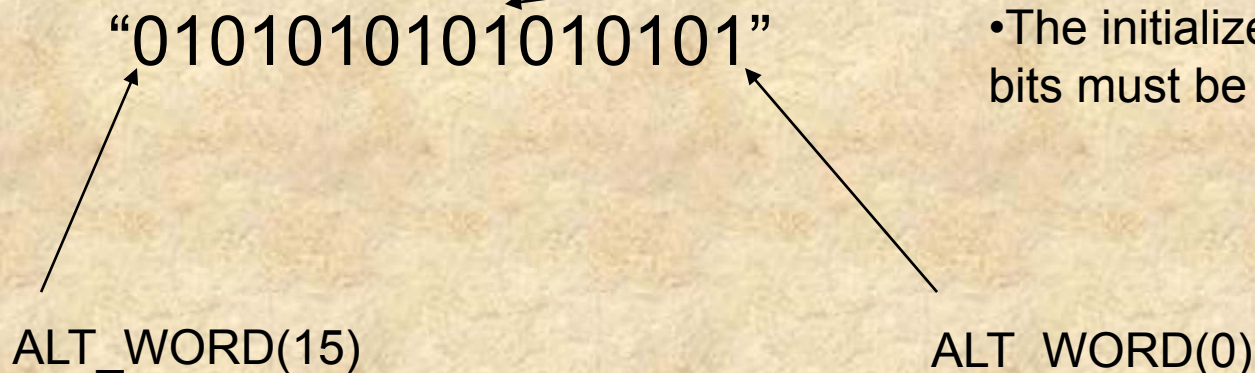- type SHORT_WORD is array (15 downto 0) of bit;
- signal DATA_WORD : SHORT_WORD; -- default value “00...0”
- signal ALT_WORD : SHORT_WORD:=“0101010101010101”;



•The initializer for an array of bits must be double quoted.

Arrays (4/11)

- Differences with arrays in Java/C++ (cont)
 - A portion of the array can be accessed in one statement
 - `ALT_WORD(5 downto 0) <= "111111";`

Arrays (5/11)

- Differences with arrays in Java/C++ (cont)
 - The slice direction must be consistent.
 - downto
 - to
 - type SHORT_WORD is array (0 to 15) of bit;
 - signal DATA_WORD : SHORT_WORD;
 - DATA_WORD (5 downto 0) <= "111111";



Wrong slice direction.

Arrays (6/11)

- Differences with arrays in Java/C++ (cont)
 - Unconstrained array types
 - type `intvec` is array (natural range <>) of integer;
 - type `matrix` is array (natural range <>
– , natural range <>) of integer;

Arrays (7/11)


- Predefined unconstrained array types in VHDL
 - type `bit_vector` is array (natural range<>) of `bit`;
 - type `String` is array (positive range <>) of `character`;

Arrays (8/11)

- Predefined unconstrained array types in VHDL
 - When declaring an array signal, the range must be specified
 - signal A: bit_vector(0 to 5) := "101011";
 - constant string1:string(1 to 29)=".....";

Arrays (9/11)

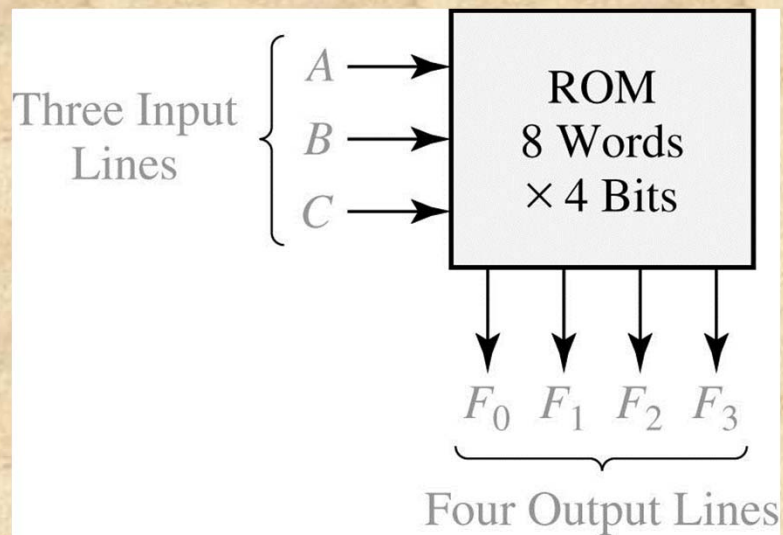- Example 1: design a ROM as illustrated in Figure 9-17.



| A | B | C | F0 | F1 | F2 | F3 |
|---|---|---|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |

Arrays (10/11)

- entity ROM9_17
- port (A,B,C: in bit; F: out bit_vector(0 to 3));
- end entity;

- or

- entity ROM9_17
- port (A: in bit_vector(0 to 2); F: out bit_vector(0 to 3));
- end entity;

Arrays (11/11)

- architecture ROM of ROM9_17 is
- type ROM8X4 is array (0 to 7) of bit_vector (0 to 3);
- constant ROM1:ROM8X4 := (“1010”, “1010”, “0111”, “0101”,
“1100”, “0001”, “1111”, “0101”);
- signal index: integer range 0 to 7;
- begin
- index <= vec2int(A&B&C); --A&B&C is a 3-bit vector
- -- vec2int is a function that converts this vector to integer
- F<=ROM1(index);
- end ROM;

VHDL Operators (1/2)

- Predefined VHDL operators

1. and or nand nor xor xnor

2. = /= < <= > >=

3. sll srl sla sra rol ror

4. + - &

5. * / mod rem

6. not abs **



Precedence

VHDL Operators (2/2)

- Predefined VHDL operators
 1. and or nand nor xor xnor
 2. = /= < <= > >=
 3. sll srl sla sra rol ror
 4. + - &
 5. * / mod rem
 6. not abs **

Packages and Libraries (1/2)

- Packages and libraries provide a convenient way of referencing frequently used functions and components
- In this class, some of your programs may need package ***bit_pack*** in library ***BITLIB***.

Packages and Libraries (2/2)

- The syntax is
 - **library BITLIB;**
 - **use BITLIB.bit_pack.all;**
- They are needed before each entity that uses library functions.