

# CDA 3200 Digital Systems

Instructor: Dr. Janusz Zalewski

Developed by: Dr. Dahai Guo

Spring 2012



# Outline

- SR Latch
- D Latch
- Edge-Triggered D Flip-Flop (FF)
- S-R Flip-Flop (FF)
- J-K Flip-Flop (FF)
- T Flip-Flop (FF)
- Flip-Flops (FFs) with Additional Inputs


# SR Latch (1/17)

- Combinational circuits
  - Outputs depend on present inputs
- Sequential circuits
  - Outputs depend on both present and the past sequence of inputs.
  - Have memory.

# SR Latch (2/17)

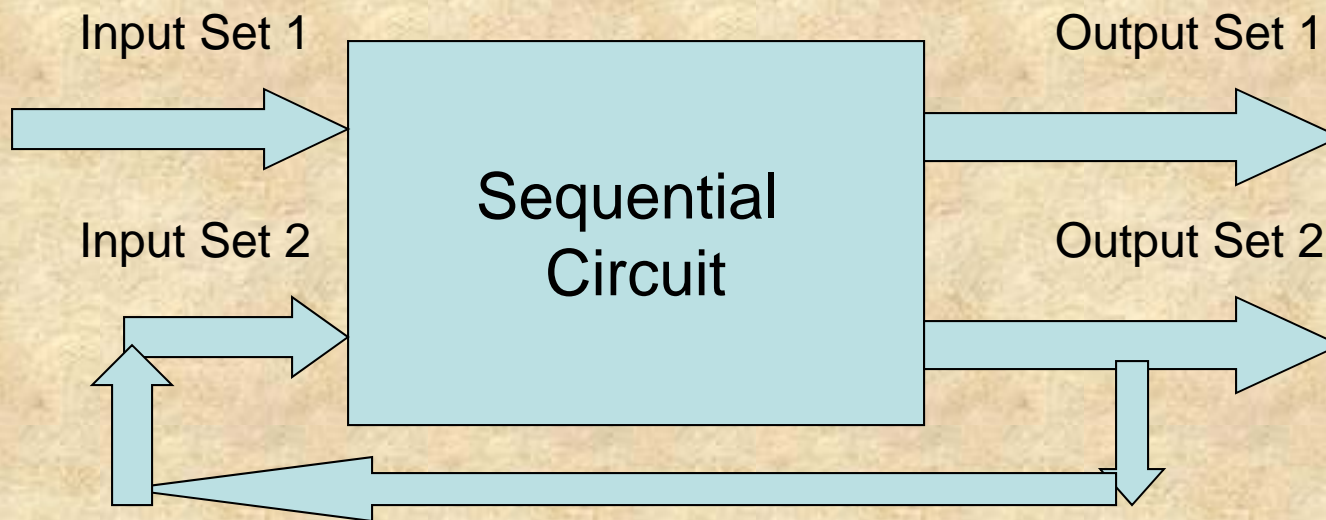 


# SR Latch (3/17)

 

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

The circuit can  
assume an initial  
and stable state:  
SR/PQ=00/10.

# SR Latch (4/17)

 


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- SR/PQ=10/01 is also stable.




# SR Latch (5/17)

 

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- SR/PQ=00/01 is also stable.

# SR Latch (6/17)

 


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- SR/PQ=01/10 is also stable.
- SR/PQ=00/10 is also stable.




# SR Latch (7/17)

 


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

# SR Latch (8/17)

 


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

# SR Latch (9/17)

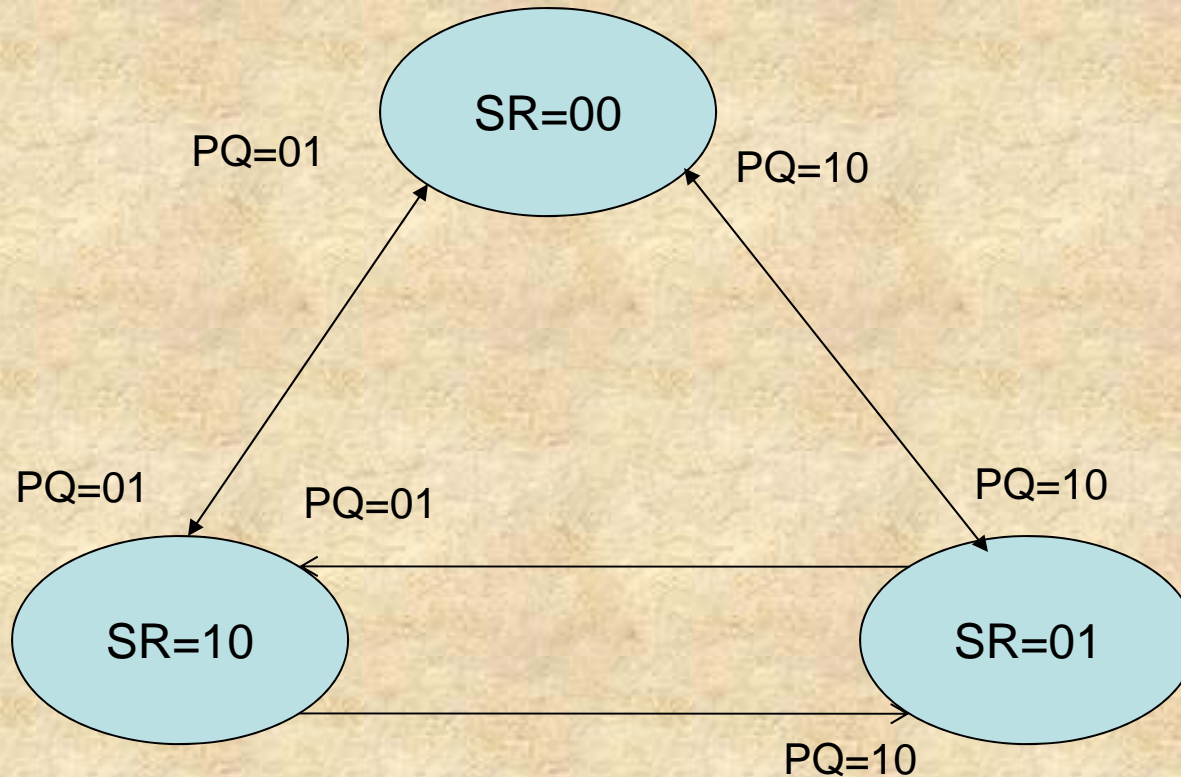

The change between any two of 00, 10, 01 will reach a stable state.

# SR Latch (10/17)

 

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

•What is PQ  
when the circuit is  
stable?

# SR Latch (11/17)



- $SR=11$  is restricted in SR latch.
- PQ cannot be both 1.

# SR Latch (12/17)

- When  $SR=10$ ,  $PQ=01$  is stable.
- When  $SR=01$ ,  $PQ=10$  is stable.
- When  $SR=00$ , both  $PQ=10$  and  $PQ=01$  are stable.
- Note
  - In the stable states,  $P=Q'$
  - Any change to  $SR=00$  will not change  $PQ$ .
  - $SR=00$  is used to keep states (remember what happened.)



# SR Latch (13/17)

 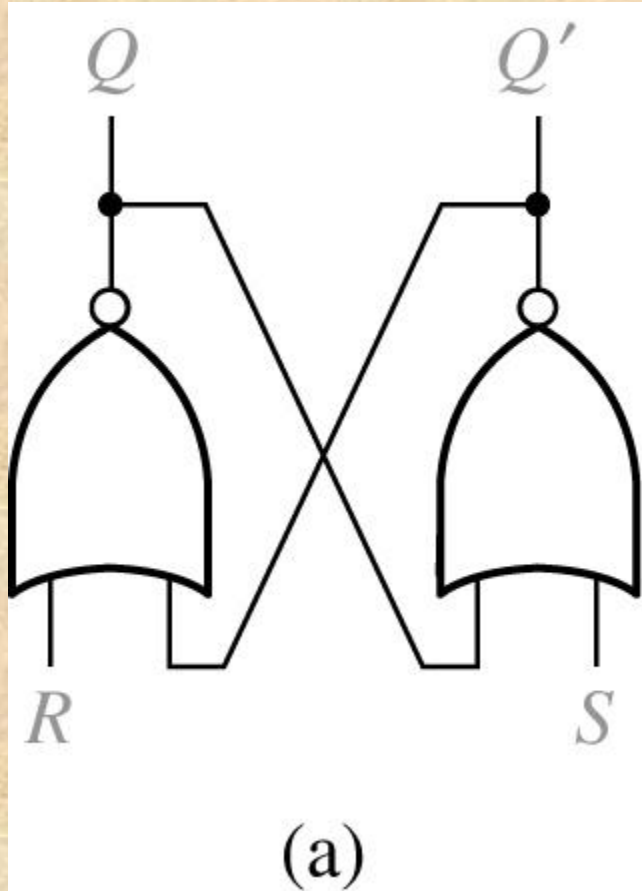

S: Set Q  
R: Reset Q

# SR Latch (14/17)

- How to draw a truth table for an SR latch?
  - Input?
  - Output?

# SR Latch (15/17)



- S R Q Q<sup>+</sup>
- 0 0 0 0
- 0 0 1 1
- 0 1 0 0
- 0 1 1 0
- 1 0 0 1
- 1 0 1 1
- 1 1 0 X
- 1 1 1 X

		$S(t)$	
		00	01
$R(t) Q(t)$	00	0	1
	01	1	1
	11	0	X
	10	0	X

$$Q(t + \epsilon) = S(t) + R'(t) Q(t)$$
  
# SR Latch (16/17)

- Alternatively, an SR latch can be realized using NAND gates.




# SR Latch (17/17)

- Alternatively, an SR latch can be realized using NAND gates.

– S-bar	R-bar	Q	Q <sup>+</sup>
– 1	1	0	0
– 1	1	1	1
– 1	0	0	0
– 1	0	1	0
– 0	1	0	1
– 0	1	1	1
– 0	0	0	X
– 0	0	1	X

# Gated D Latch (1/3)

 

- What are  $S$  and  $R$  when  $G=0$ ?
- $G=0$  keeps states:  $Q^+=D$ .
- Can  $SR=11$  ever occur?
- $Q^+=D$  when  $G=1$ .



# Gated D Latch (2/3)

$Q$ \ $GD$	00	01	11	10
0	0	0	1	0
1	1	1	1	0

$Q^+ = G'Q + GD$


- No “do not care” terms.

# Gated D Latch (3/3)

- `if(G==1){`
- `Q+ = D;`
- `}else{`
- `Q+ = Q;`
- `}`

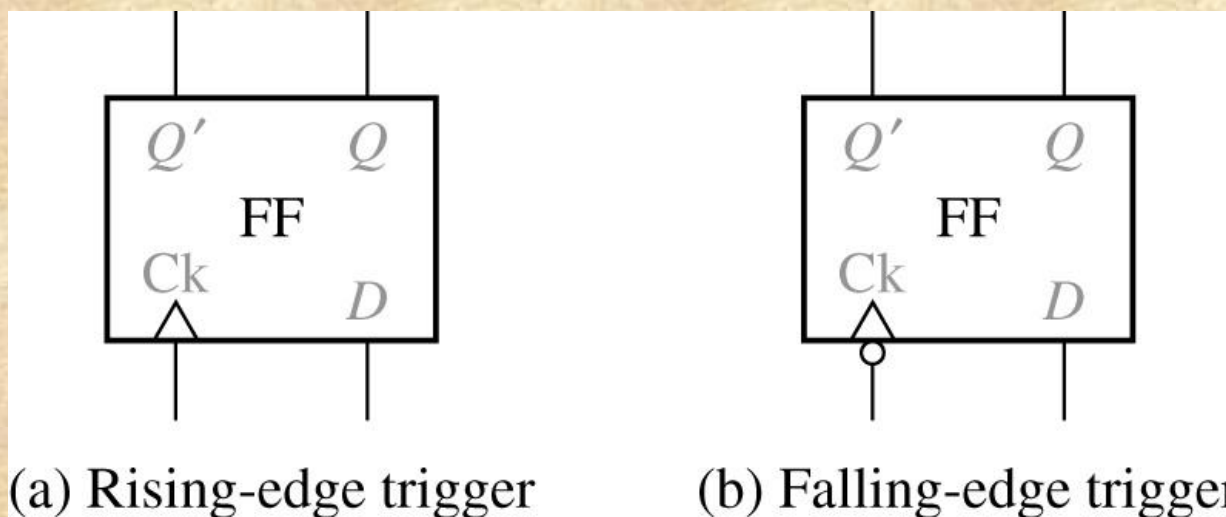
# Edge-Triggered D Flip-Flop (FF) (1/3)

- If the G signal in the D latch is connected to a clock input, the output changes only in response to the clock, not to a change in D.
- And we call this latch a D Flip-Flop (FF).




$$Q^+ = D$$

## Edge-Triggered D Flip-Flop (FF) (2/3)

 

 
(a) Construction from two gated D latches



(b) Time analysis

# Edge-Triggered D Flip-Flop (FF) (3/3)


Note Q does not change during  $Ck=0$ .

 

- Timing for D Flip-Flops  
(FF) (Falling-Edge Trigger)

 
# S-R Flip-Flop (FF) (1/3)

- $Q^+$  changes in response to the clock signal.






# S-R Flip-Flop (FF) (2/3)

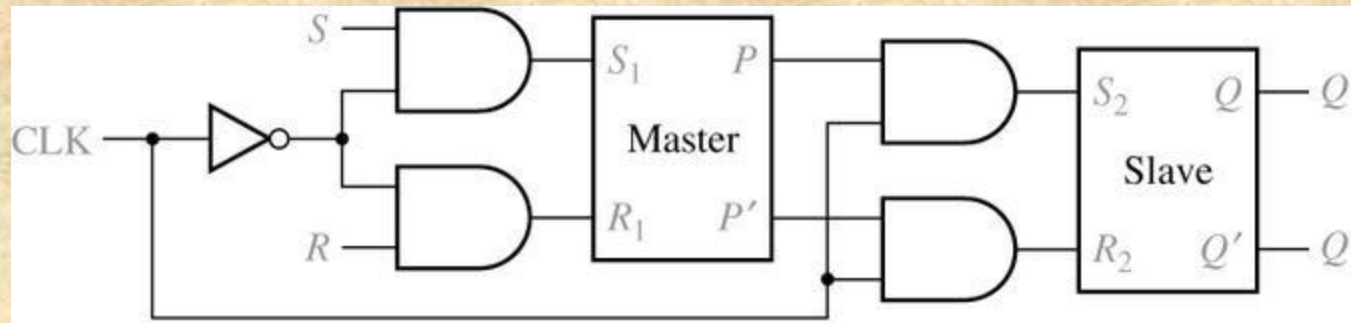

(a) Implementation with two latches

 

(b) Timing analysis

- When CLK=0
  - $P^+ = S_1 + R_1'P$
- When CLK=1
  - $Q^+ = P$

# S-R Flip-Flop (FF) (3/3)

- Why master-slave Flip-Flops (FFs)?
  - The master Flip-Flop (FF) holds the output for in the first half clock cycle.
  - When the slave Flip-Flop (FF) updates and outputs, the master is closed.
  - This mechanism guarantees that the final output changes only once in a clock cycle.


# JK Flip-Flop (FF) (1/2)

- An extended version of the SR Flip-Flop (FF)
  - J corresponds to S
  - K corresponds to R

• J	K	Q	Q <sup>+</sup>
• 0	0	0	0
• 0	0	1	1
• 0	1	0	0
• 0	1	1	0
• 1	0	0	1
• 1	0	1	1
• 1	1	0	1
• 1	1	1	0

JK can be 11. This configuration changes the state of Q.


# JK Flip-Flop (FF) (2/2)

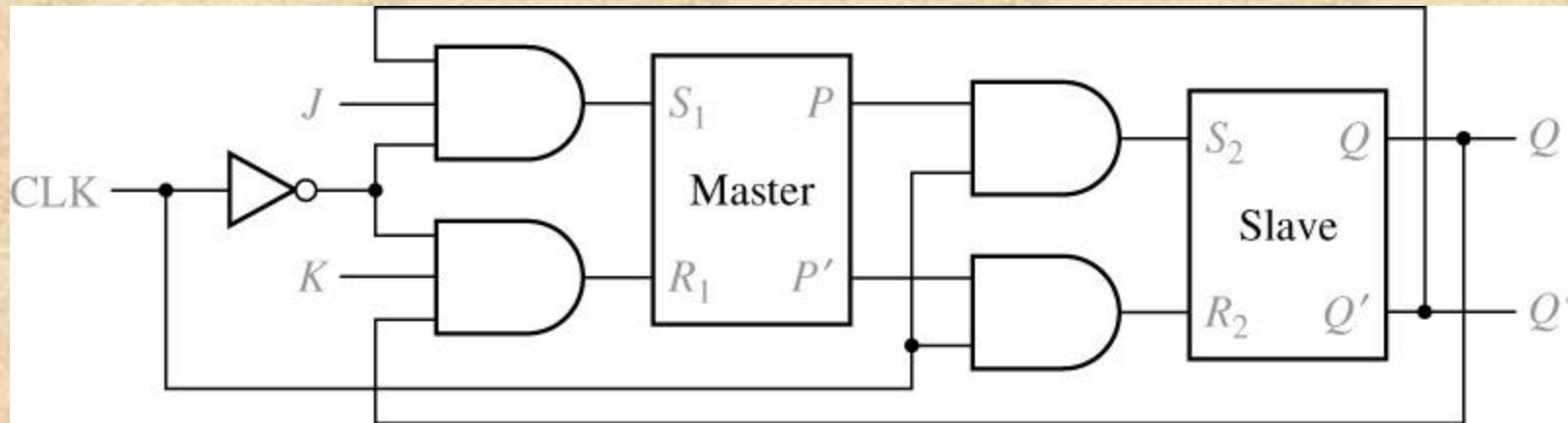

- $S_1 = J * Q' * CLK'$
- $R_1 = K * Q * CLK'$
- S1 and R1 cannot be 1 at the same time.
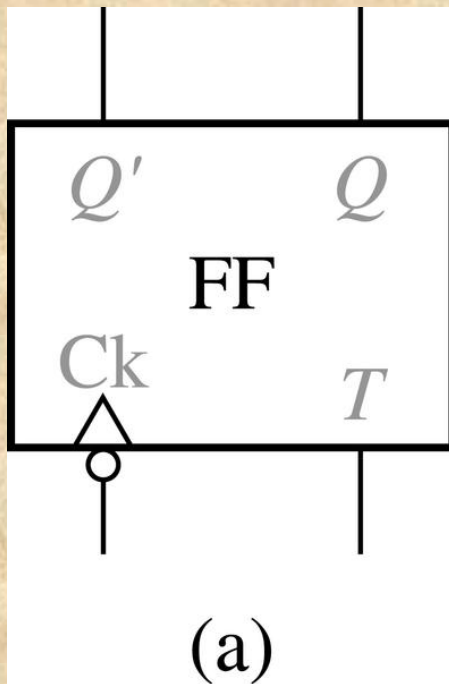
# T Flip-Flop (FF) (1/2)

- $T=0 \rightarrow$  no state change
- $T=1 \rightarrow$  state changes




T	Q	Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0


$$Q^+ = T \text{ xor } Q$$



# T Flip-Flop (FF) (2/2)

 

(a) Conversion of J-K to  $T$

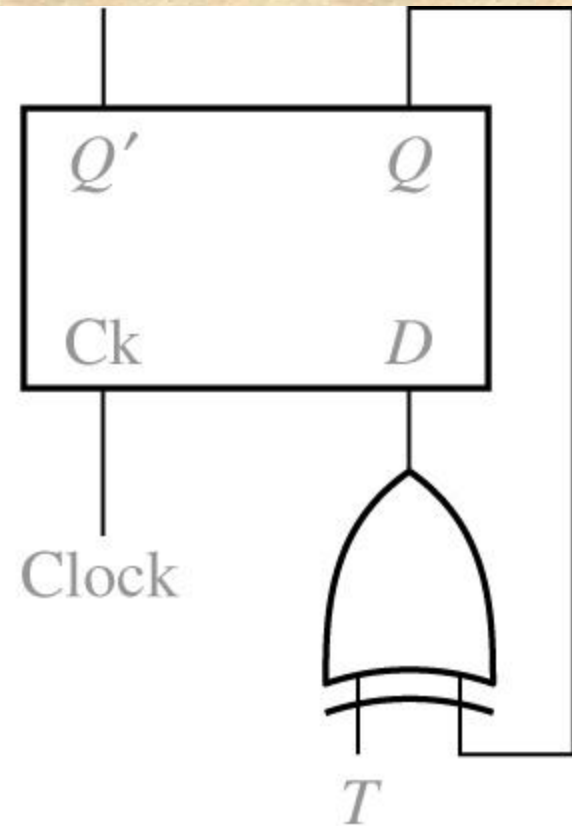

(b) Conversion of  $D$  to  $T$



# Summary (1/8)


- All the Flip-Flops (FFs) and D latch are based on **SR** latch.
- **SR** latch can be described using
  - $Q^+ = S + R'Q$
  - $S=1$  sets  $Q$
  - $R=1$  resets  $Q$
  - $SR=00$  keeps states ( $Q$  does not change.)

# Summary (2/8) $Q^+ = S + R'Q$

- Gated D latch
  - $S = DG$
  - $R = D'G$
  - When  $G=0$ ,  $SR=00 \rightarrow$  state kept.
  - When  $G=1$ ,  $Q=D$ 
    - When  $D=0$ ,  $SR=01 \rightarrow$  reset  $Q \rightarrow$   $Q=0$
    - When  $D=1$ ,  $SR=10 \rightarrow$  set  $Q \rightarrow$   $Q=1$

 
# Summary (3/8) $Q^+ = S + R'Q$

- When G is a clock signal, two gated D latches comprise an edge-triggered D Flip-Flop (FF)




if(CLK is low)  
Q does not  
change  
else  
Q becomes D  
shortly after  
the rising  
edge

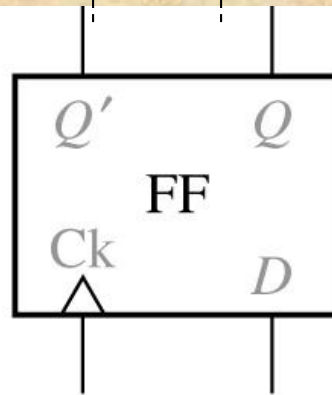- Note Q's waveform is not exactly the same with D's.



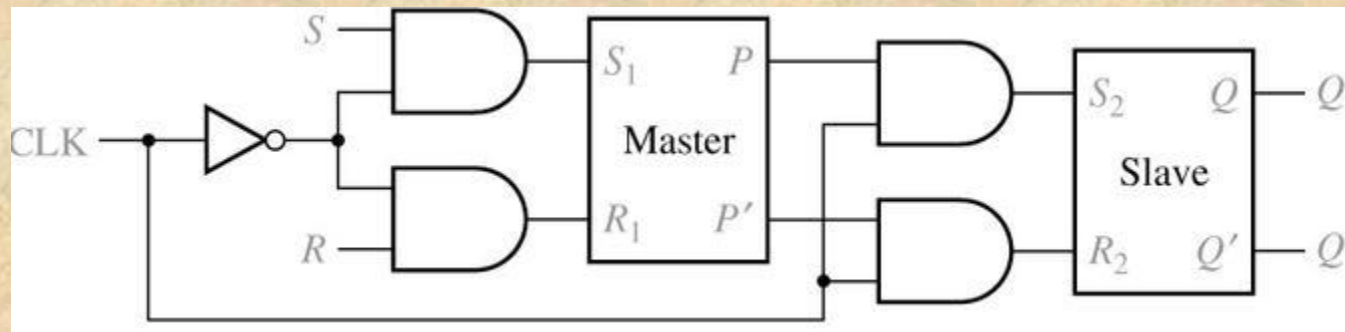
# Summary (4/8) $Q^+ = S + R'Q$

- SR Flip-Flop (FF)
  - Master and slave
  - When the master receives the input and updates, the slave is close.
  - When the slave outputs, the master does not respond to any input change.


 
# Summary (5/8) $Q^+ = S + R'Q$


- SR Flip-Flop (FF) (cont)
  - When CLK is low,
    - $S_1R_1 = SR \rightarrow P^+ = S + R'P$ , master is updated
    - $S_2R_2 = 00 \rightarrow Q$  does not change




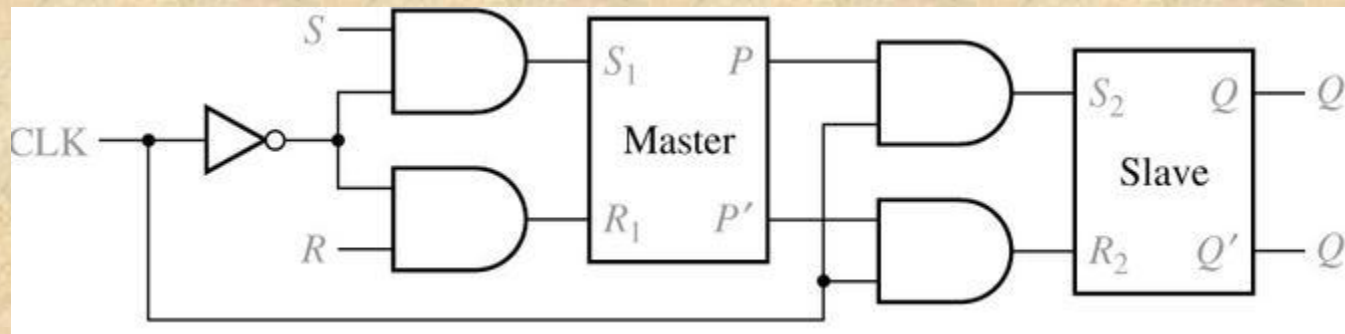
# Summary (6/8) $Q^+ = S + R'Q$


- SR Flip-Flop (FF) (cont)
  - When CLK is high,
    - $S_1R_1=00 \rightarrow P$  does not change
    - master does not respond to inputs
    - $S_2R_2=PP' \rightarrow Q^+ = P + (P')'Q = P$





# Summary (7/8) $Q^+ = S + R'Q$

- SR Flip-Flop (FF) (cont)

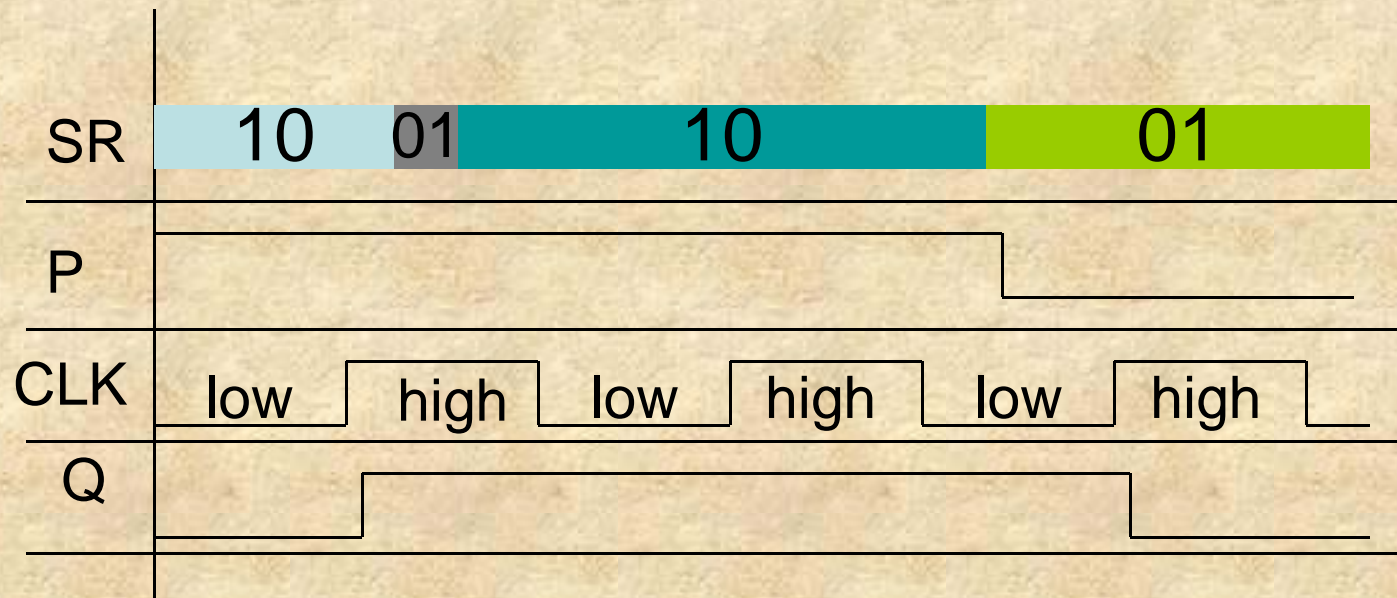

- Master

- Slave


- The final output, Q, was not affected by 01 .

# Summary (8/8) $Q^+ = S + R'Q$


- JK Flip-Flop (FF)
  - Very similar to SR master-slave Flip-Flop (FF)
  - Except JK=11 inverts the output
- T Flip-Flop (FF)
  - T=1 → inverts the output
  - T=0 → keeps the same output
 
# Flip-Flops (FFs) with Additional Inputs (1/3)

- Clear and Preset signals are two asynchronous signals and do not depend on CLK.


 
# Flip-Flops (FFs) with Additional Inputs (2/3)



# Flip-Flops (FFs) with Additional Inputs (3/3)

- Clock enable signal

