

CDA 3200 Digital Systems

Instructor: Dr. Janusz Zalewski

Developed by: Dr. Dahai Guo

Spring 2012

Outline

- A Sequential Parity Checker
- “01” Detector
- Analysis by Signal Tracing and Timing Charts

A Sequential Parity Checker (1/13)


- Parity bit is used to detect errors.

– Example:

• 7 data bits	parity bits
• 0000000	0
• 0000001	1
• 0110110	0
• 1010101	1
• 0111000	1

A Sequential Parity Checker (2/13)

 - Parity checker
 - A group of bits is applied to X
 - Z indicates the parity.




A Sequential Parity Checker (3/13)

- Goals
 - Decide how many flip-flops (FFs) are needed
 - Decide the expressions for flip-flop (FF) inputs
 - Decide the expression for the final output
- Tools
 - Time waveform
 - State graph
 - State table


A Sequential Parity Checker (4/13)

 - Time waveform
 - Can help us understand the problem.
 - But cannot help in developing logic expressions.



A Sequential Parity Checker (5/13)

 
- State graph
 - States are independent of circuit realization.
 - They reflect what've happened and maybe also indicate the output.



State zero, where the output is zero.

A Sequential Parity Checker (6/13)

 - In a parity checker, only two states are needed.
 - S_0 : even number of 1's have been received.
 - S_1 : odd number of 1's have been received.



All possible transitions have been considered.

A Sequential Parity Checker (7/13)

- State table
 - Can be realization-free.

Present State	Next State		Present Output (Z)
	X=0	X= 1	
S ₀	S ₀	S ₁	0
S ₁	S ₁	S ₀	1

A Sequential Parity Checker (8/13)

- State table (cont)
 - Two states can be represented by 1 bit.

Present State	Next State		Present Output (Z)
	X=0	X= 1	
S ₀ 0	S ₀ 0	S ₁ 1	0
S ₁ 1	S ₁ 1	S ₀ 0	1

A Sequential Parity Checker (9/13)

- State table (cont)
 - Say we are using a T flip-flop (FF) ($Q^+ = Q \text{ xor } T$)

Present State Q	Next State Q^+		Present Output (Z)
	X=0	X=1	
0	0	1	0
1	1	0	1

How can we decide T's?

A Sequential Parity Checker (10/13)

- State table (cont)
 - Say we are using a T flip-flop (FF) ($Q^+ = Q \text{ xor } T$)

Q	Q ⁺ / T		Present Output (Z)
	X=0	X= 1	
0	0 / 0	1 / 1	0
1	1 / 0	0 / 1	1

A Sequential Parity Checker (11/13)

- State table (cont)

– What is the expression for T? $T=X$

Q	Q ⁺ / T		Present Output (Z)
	X=0	X=1	
0	0 / 0	1 / 1	0
1	1 / 0	0 / 1	1

A Sequential Parity Checker (12/13)

- State table (cont)


- What is the expression for Z?

$$Z=Q$$

Q	Q ⁺ / T		Present Output (Z)
	X=0	X= 1	
0	0 / 0	1 / 1	0
1	1 / 0	0 / 1	1

A Sequential Parity Checker (13/13)

- Parity check

 


“01” Detector (1/10)

- Detects bit pattern “01” in a serial input
 - Input: 0111110100
 - Output: 0100000100

“01” Detector (2/10)

- State graph
 - We do not necessarily know how many states are needed ahead of time.
 - We can assume an initial state which is before any input.
 - Then there will be two transitions from the initial state and they are triggered by 0 and 1.
 - A transition may introduce a new state.

“01” Detector (3/10)

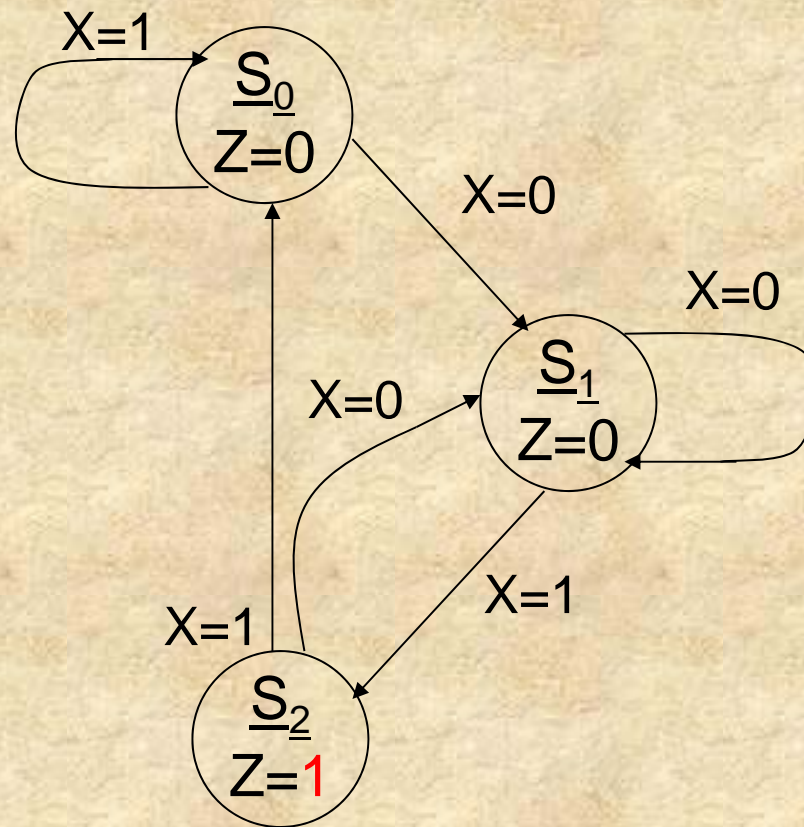

“01” Detector (4/10)

- S_0 : nothing has been received to make a “01”.
- S_1 : “0” has been received.
- S_2 : “01” has been received.

How many bits are needed to represent S_{0-2} ?

“01” Detector (5/10)

- State table

Present State	Next State		Present Output (Z)
	X=0	X= 1	
S_0	S_1	S_0	0
S_1	S_1	S_2	0
S_2	S_1	S_0	1

“01” Detector (6/10)

- State table (cont)
 - Encode states
 - S_0 : 00
 - S_1 : 01
 - S_2 : 10

“01” Detector (7/10)

- State table (cont)

$Q_1 Q_0$ Present State	Next State		Present Output (Z)
	X=0	$Q_1^+ Q_0^+$ X= 1	
S_0 00	S_1 01	S_0 00	0
S_1 01	S_1 01	S_2 10	0
S_2 10	S_1 01	S_0 00	1

“01” Detector (8/10)

- State table (cont): T flip-flops (FFs) are used

Q_1Q_0	$Q_1^+ Q_0^+ / T_1 T_0$		Present Output (Z)
	$X=0$	$X=1$	
00	01/ 01	00/ 00	0
01	01/ 00	10/ 11	0
10	01/ 11	00/ 10	1

Note:
variables
are Q_1 ,
 Q_0 , and
 X ?

“01” Detector (9/10)

- What are the expressions for T_1 , T_0 , & Z ?

Q_1Q_0	$Q_1^+ Q_0^+ / T_1 T_0$ $X=0$	$X=1$	Present Output (Z)
00	01/ 01	00/ 00	0
01	01/ 00	10/ 11	0
10	01/ 11	00/ 10	1

Note:
variables
are Q_1 ,
 Q_0 , and
 X ?

“01” Detector (10/10)

•	Q_1	Q_0	X	T_1	T_0	Z
•	0	0	0	0	1	0
•	0	0	1	0	0	0
•	0	1	0	0	0	0
•	0	1	1	1	1	0
•	1	0	0	1	1	1
•	1	0	1	1	0	1
•	1	1	0	X	X	X
•	1	1	1	X	X	X

Minterms → expressions!!



Analysis by Signal Tracing and Timing Charts (1/6)

- Moore machine
 - The output depends only on the present state of the flip-flops (FFs).
 - $Z = F(Q_n, Q_{n-1}, \dots, Q_1, Q_0)$
- Mealy machine
 - The output depends not only on the present state, but also the value of the circuit inputs.
 - $Z = F(Q_n, Q_{n-1}, \dots, Q_1, Q_0, X_m, X_{m-1}, \dots, X_1, X_0)$

Analysis by Signal Tracing and Timing Charts (2/6)

- Because flip-flops (FFs) only respond to input at rising/falling edges, the output of a **Moore** machine only changes at rising/falling edges.

 
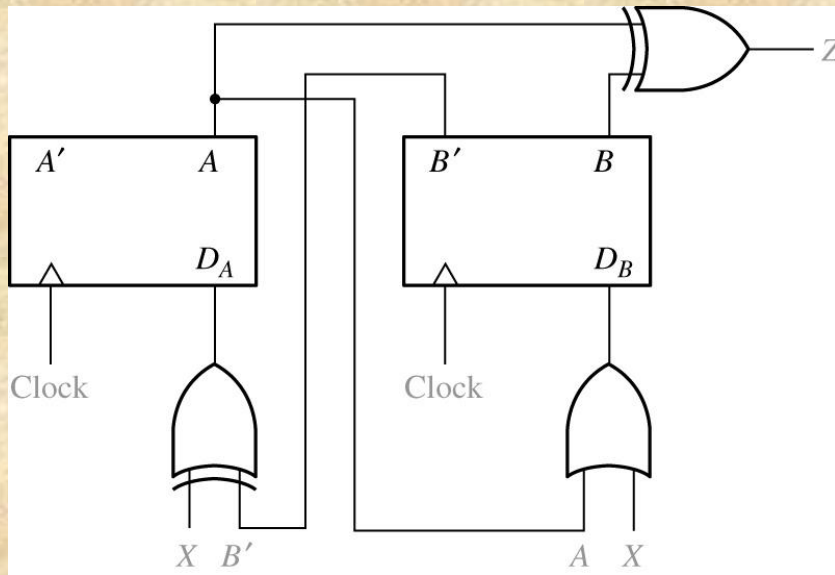
Analysis by Signal Tracing and Timing Charts (3/6)



Analysis by Signal Tracing and Timing Charts (4/6)

- In a Mealy machine, outputs changes when flip-flops (FFs) and/or circuit input change.
- Therefore, when the circuit output changes is independent of rising/falling edges.

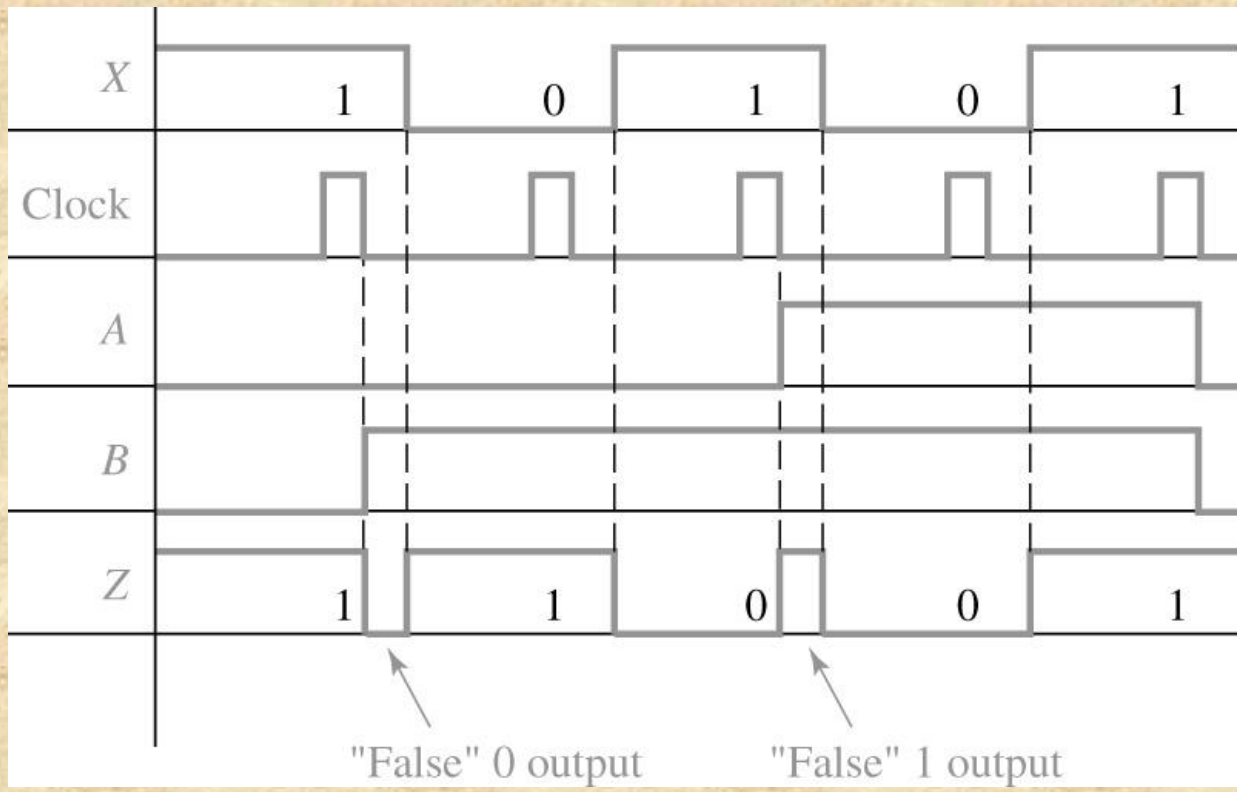 Analysis by Signal Tracing and Timing Charts (5/6)



Analysis by Signal Tracing and Timing Charts (6/6)

- In a Mealy machine, the output is read immediately before the rising/falling edge.

