

CDA 3200 Digital Systems

Instructor: Dr. Janusz Zalewski

Developed by: Dr. Dahai Guo

Spring 2012

Outline

- Combinational Logic Design Using a Truth Table
- Minterm and Maxterm Expansions
- General Minterm and Maxterm Expansions
- Incompletely Specified Functions
- Examples of Truth Table Construction
- Design of Binary Adders and Subtractors

Combinational Logic Design Using a Truth Table (1/5)

- Sometimes, it is easier to first construct a truth table before developing the logic expression and design the logic circuit.
- The logic expression can be written in form of sum-of-products or product-of-sums, depending on how to interpret the truth table.

Combinational Logic Design Using a Truth Table (2/5)

- Any combination of 011, 100, 101, 110 or 111 can make $f=1$
 - ABC are 011 $\rightarrow A'BC=1$
 - ABC are 100 $\rightarrow AB'C'=1$
 - ABC are 101 $\rightarrow AB'C=1$
 - ABC are 110 $\rightarrow ABC'=1$
 - ABC are 111 $\rightarrow ABC=1$

A	B	C	<i>dec</i>	f	f'
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	1	0
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	0

Combinational Logic Design Using a Truth Table (3/5)

- Therefore, the logic expression is
 - $f = A'BC + AB'C' + AB'C + ABC' + ABC$
 - $= A'BC + AB' + AB$
 - $= A'BC + A$
 - $= (A' + A)(A + BC)$
 - $= A + BC$

Combinational Logic Design Using a Truth Table (4/5)

- Any combination of 000, 001, or 010 can make $f'=1$
 - ABC are 000 $\rightarrow A'B'C'=1$
 - ABC are 001 $\rightarrow A'B'C=1$
 - ABC are 010 $\rightarrow A'BC'=1$

A	B	C	<i>dec</i>	f	f'
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	1	0
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	0

Combinational Logic Design Using a Truth Table (5/5)

- Therefore, the logic expression for f' is
 - $f' = A'B'C' + A'B'C + A'BC'$
 - $(f')' = (A'B'C' + A'B'C + A'BC)'$
 - $f = (A'B'C')'(A'B'C)'(A'BC)'$
 - $= (A+B+C)(A+B+C')(A+B'+C)$

Minterm and Maxterm Expansions (1/10)

- A literal is a variable or its complement.
- A minterm of n variables is a product of n literals in which each variable appears once in either true or complemented form, but not both.
 - For a system with 3 variables
 - ABC is a minterm
 - AB'C' is a minterm
 - A'C' is NOT a minterm

Minterm and Maxterm Expansions (2/10)

- A minterm is designated m_i , where i is the decimal value of the binary string of the variables.

– ABC m_7

– A'B'C' m_0

– ABC' m_6

Minterm and Maxterm Expansions (3/10)

- The truth table of a logic function can be represented by a sum of minterms and in this case it is called a minterm expansion or a standard sum of products

Minterm and Maxterm Expansions (4/10)

- $f = A'BC + AB'C' + AB'C + ABC' + ABC$
- $f = m_3 + m_4 + m_5 + m_6 + m_7$
- $f(A,B,C) = \sum m(3,4,5,6,7)$

A	B	C	<i>dec</i>	f	f'
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	1	0
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	0

Minterm and Maxterm Expansions (5/10)

- Given a truth table, if the output of a certain row is 1, the corresponding minterm must be present in the logic expression.

Minterm and Maxterm Expansions

(6/10)

- A maxterm of n variables is a sum of n literals.
 - In a system with three variables
 - $(A+B+C)$ is a maxterm
 - $(A'+B'+C)$ is a maxterm
 - $(A'+B)$ is not maxterm
- A maxterm is designated M_i , where i is the decimal value of the complement of the binary string.

Minterm and Maxterm Expansions (7/10)

- $f=(A+B+C)(A+B+C')(A+B'+C)$
- $f=M_0M_1M_2$
- $f= \prod M(0,1,2)$

A	B	C	<i>dec</i>	f	f'
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	1	0
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	0

Minterm and Maxterm Expansions (8/10)

- Converting a general logic expression into a minterm expansion
 - Through repeatedly applying $X+X'=1$
 - $f=a'b'+a'd+acd'$
 - $=a'b'(c+c')(d+d')+a'd(b+b')(c+c')+acd'(b+b')$
 - $=a'b'c'd'+a'b'c'd+a'b'cd'+a'b'cd+a'bcd+a'bcd+abcd'+ab'cd'$
 - Note: a minterm expression is not necessarily the simplest expression.

Minterm and Maxterm Expansions (9/10)

- Converting a general logic expression into a maxterm expression
 - Through repeatedly applying $XX'=0$

Minterm and Maxterm Expansions (10/10)

- When comparing two logic expressions, you can convert both into their minterm expressions and then compare.
 - Example:
 - $a'c + b'c' + ab$ and $a'b' + bc + ac'$

General Minterm and Maxterm Expansion (1/3)

- A minterm expansion for an n variable function can be represented as a 2^n long vector
 - Example:
 - $F(A,B,C) = a_0m_0 + a_1m_1 + \dots + a_6m_6 + a_7m_7 = \sum_{i=0}^7 a_i m_i$
 - If $a_i=1$, m_i is present in the expression.

General Minterm and Maxterm Expansion (2/3)

- Similarly, a maxterm expansion for an n variable function can also be represented as a 2^n long vector

- $F(A,B,C) = (a_0 + M_0)(a_1 + M_1)...(a_6 + M_6)(a_7 + M_7) = \prod_{i=0}^7 (a_i + M_i)$

- If a_i is 0, M_i is present in the expression. Why?

General Minterm and Maxterm Expansion (3/3)

- Given two different minterm expansions of n variables

$$f_1 = \sum_{i=0}^{2^n-1} a_i m_i$$

$$f_2 = \sum_{j=0}^{2^n-1} b_j m_j$$

$$f_1 f_2 = \left(\sum_{i=0}^{2^n-1} a_i m_i \right) \left(\sum_{j=0}^{2^n-1} b_j m_j \right) = \sum_{i=0}^{2^n-1} \sum_{j=0}^{2^n-1} a_i b_j m_i m_j = \sum_{i=0}^{2^n-1} a_i b_i m_i$$

Incompletely Specified Functions (1/5)

- Sometimes, not all the combinations of the inputs are considered in the circuit.
- Unconsidered combinations are referred to as “do not care” terms.
- In the truth table, the outputs for “do not care” terms are designated ‘X’

Incompletely Specified Functions (2/5)

- We could ignore the “do not care” terms, then the logic expression is
- $F = A'B'C' + A'BC + ABC$
- $= A'B'C' + BC$

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

Incompletely Specified Functions (3/5)

- It does not matter, if we assign 1/0 to Xs
 - $F = A'B'C' + BC + A'B'C$
 - $= A'B' + BC$ Simpler expression

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Incompletely Specified Functions (4/5)

- Sometimes, assigning 1 to X's may contribute to simplifying the logic expression.

Incompletely Specified Functions (5/5)

- In a minterm expansion, the “do not care” terms are denoted ***d***

$$F = \sum m(0,3,7) + \sum d(1,6)$$


- In a maxterm expansion, the “do not care” terms are denoted ***D***

$$F = \prod M(2,4,5) + \prod D(1,6)$$

Design of Binary Adders and Subtractors (1/7)

- Full Adders

X	Y	C_{in}	Dec	C_{out}	Sum
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	0	1
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	1

 

$$C_{out} = m_3 + m_5 + m_6 + m_7$$

$$Sum = m_1 + m_2 + m_4 + m_7$$

Design of Binary Adders and Subtractors (2/7)

- $\text{Sum} = m_1 + m_2 + m_4 + m_7$

- $\text{Sum} = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$

- $= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in})$

- $= X'(Y \text{ xor } C_{in}) + X(Y \text{ xor } C_{in})'$

- $= X \text{ xor } (Y \text{ xor } C_{in}) = X \text{ xor } Y \text{ xor } C_{in}$

- $C_{out} = m_3 + m_5 + m_6 + m_7$

- $C_{out} = X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in}$


- $= YC_{in} + XC_{in} + XY$

Design of Binary Adders and Subtractors (3/7)

Full Adder


$$\text{Sum} = X \text{ xor } Y \text{ xor } C_{\text{in}}$$
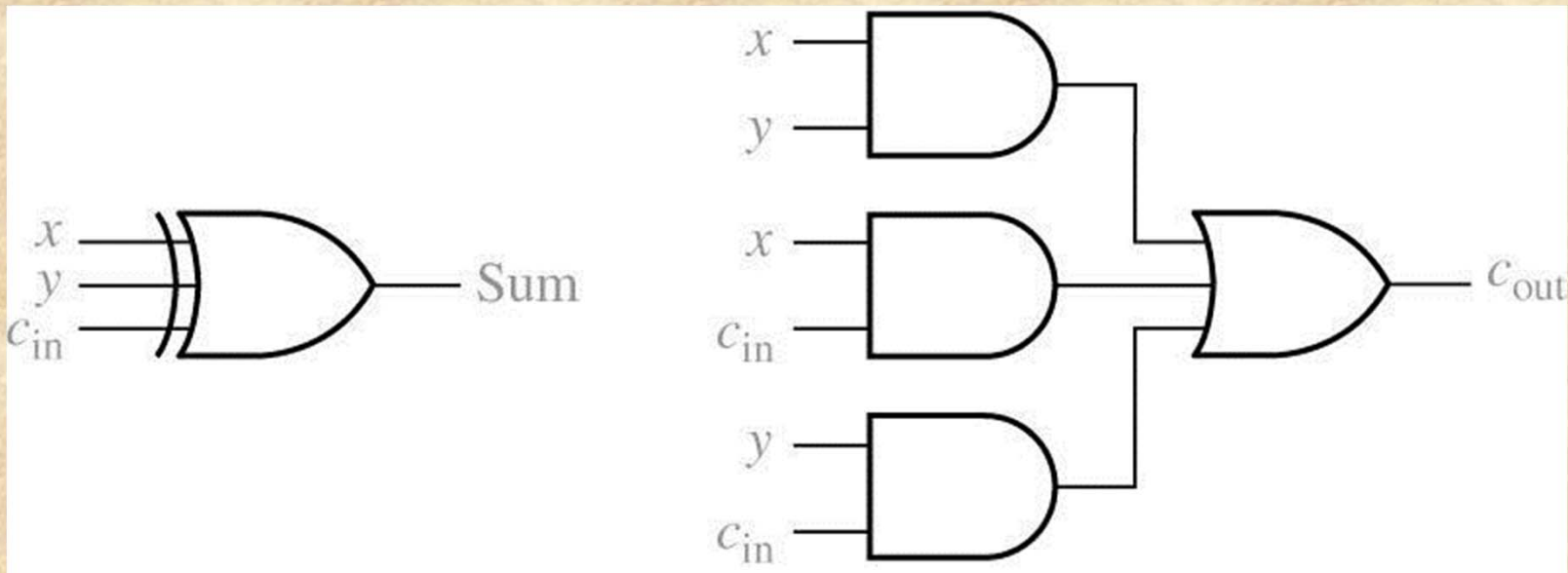
$$C_{\text{out}} = YC_{\text{in}} + XC_{\text{in}} + XY$$



Design of Binary Adders and Subtractors (4/7)

 - Four full adders can be used to make a 4-bit binary adder



Design of Binary Adders and Subtractors (5/7)

- When adding two signed number, overflow must be considered.
 - Adding two positive numbers gives a negative number: $A_3B_3S_3'$
 - Adding two negative numbers gives a positive number: $A_3'B_3'S_3$
 - $V=A_3'B_3'S_3+A_3B_3S_3'$ can be used to reflect if overflow occurs

Design of Binary Adders and Subtractors (6/7)

- Binary subtractor using full adders
 - Remember two's complement
 - Reverse all the bits
 - Add 1

Design of Binary Adders and Subtractors (7/7)

