

CDA 3200 Digital Systems

Instructor: Dr. Janusz Zalewski

Developed by: Dr. Dahai Guo


Spring 2012

Outline

- Multiplexers
- Three-State Buffers
- Decoders and Encoders
- Read-Only Memories
- Programmable Logic Devices


Multiplexers (1/4)

 - A multiplexer (MUX) has a group of data inputs and a group of control inputs.
- The control inputs are used to select one of the data inputs.



$A=0 \rightarrow Z=I_0$
 $A=1 \rightarrow Z=I_1$

Multiplexers (2/4)

 



- $Z_{4\text{-to-}1} = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$
- $Z_{8\text{-to-}1} = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$

Multiplexers (3/4)

- n control inputs can select 2^n inputs.
- The logic expression for an n-control-input MUX is $Z = \sum_{k=0}^{2^n-1} m_k I_k$, where m_k is the minterm whose decimal representation is k

Multiplexers (4/4)

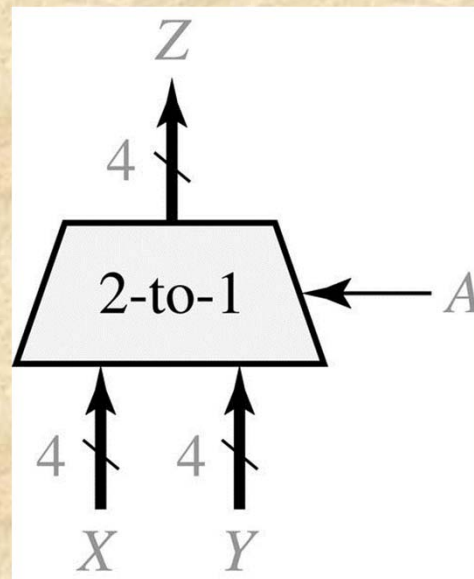 
- Several multiplexers can be used to select from binary numbers.



Bus Inputs/Outputs

Three-State Buffers (1/5)

 
- A three-state buffer has an enable input



B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

The symbol Z represent the buffer is in the high-impedance (Hi-Z) state.


Three-State Buffers (2/5)

 

B	A	C	B	A	C	B	A	C	B	A	C
0	0	Z	0	0	Z	0	0	0	0	0	1
0	1	Z	0	1	Z	0	1	1	0	1	0
1	0	0	1	0	1	1	0	Z	1	0	Z
1	1	1	1	1	0	1	1	Z	1	1	Z


Three-State Buffers (3/5)

 - How to use three-state buffers to realize a 2-to-1 multiplexer?




Three-State Buffers (4/5)

 - 4-bit adder with four sources for one operand.



Three-State Buffers (5/5)


- Bi-Directional input/output pin.

 

EN=1: Output
EN=0: Input

Decoders and Encoders (1/3)


- Example: a 3-to-8 decoder.

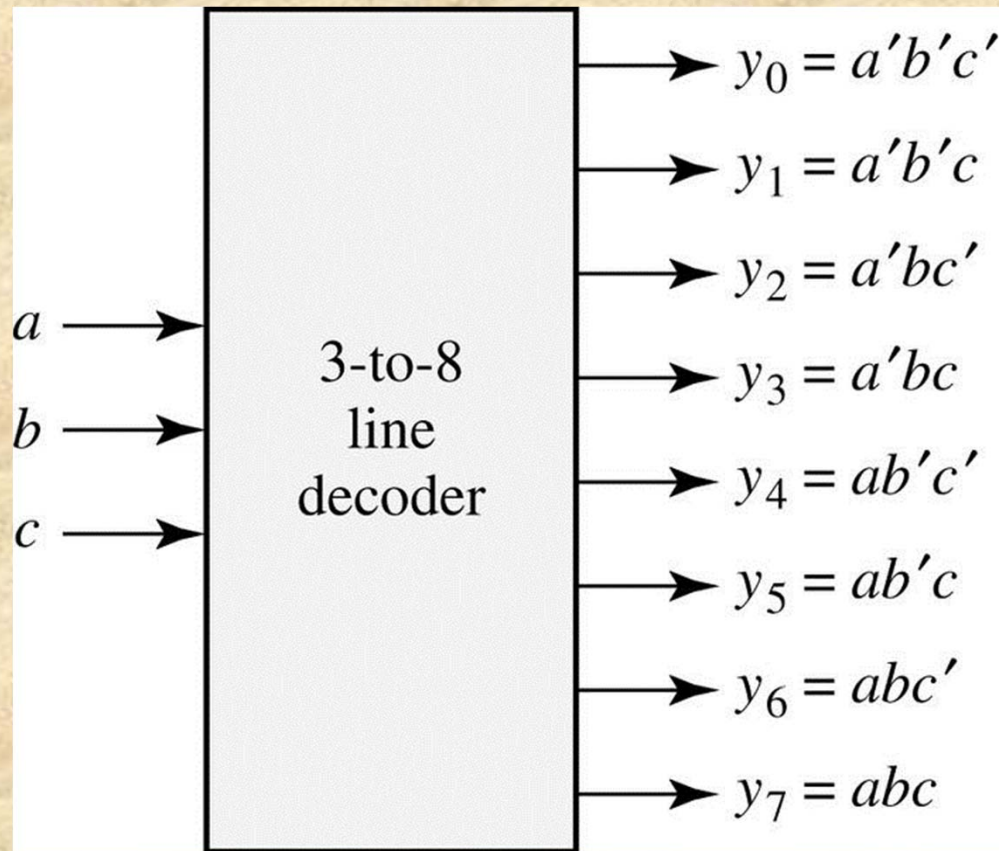

Only the output whose subscript is equal to the binary number: abc is 1.

Decoders and Encoders (2/3)


- Example 2: a 4-to-10 decoder

 

Only the output, whose subscript is equal to the binary number: ABCD, is 0.

Decoders and Encoders (3/3)

- Example 3: 8-to-3 priority encoder

 


If none of y_0 - y_7 is 1, d is 0; otherwise, the binary number abc indicates the highest numbered input whose value is 1.

Read-Only Memories (1/6)

- ROM: read-only memory
 - Interconnected gates to store an array of binary data
 - Inputs serve as address
 - Stored data cannot be changed under normal operating conditions

Read-Only Memories (2/6)

- Example 1:

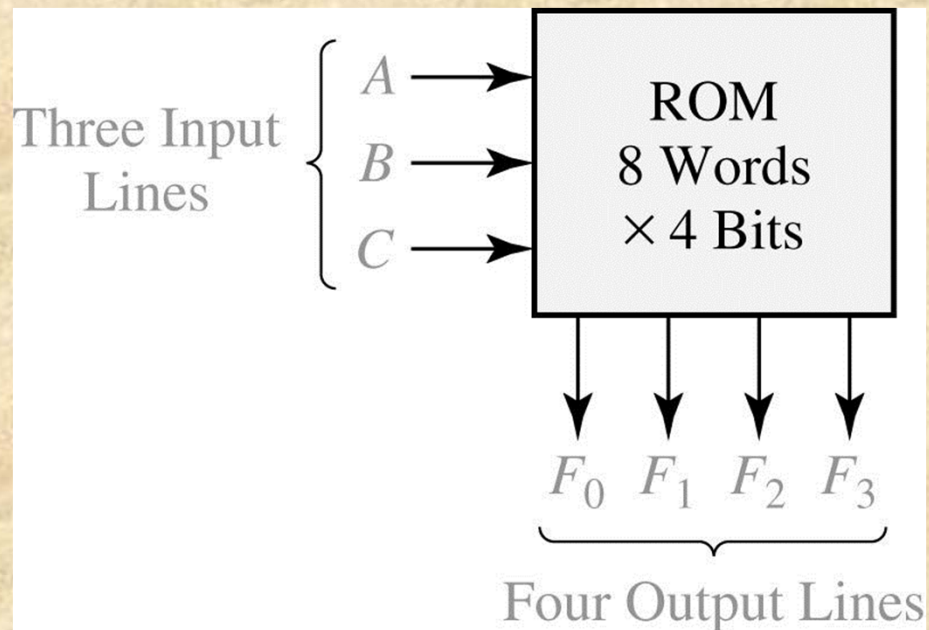


A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

Read-Only Memories (3/6)

- $F_0 = \text{sum}[m(0,1,4,6)] = A'B' + AC'$
- $F_1 = \text{sum}[m(2,3,4,6,7)] = B + AC'$
- $F_2 = \text{sum}[m(0,1,2,6)] = A'B' + BC'$
- $F_3 = \text{sum}[m(2,3,5,6,7)] = AC + B$
- Then, we can realize these expressions using an AND-OR network.

Read-Only Memories (4/6)

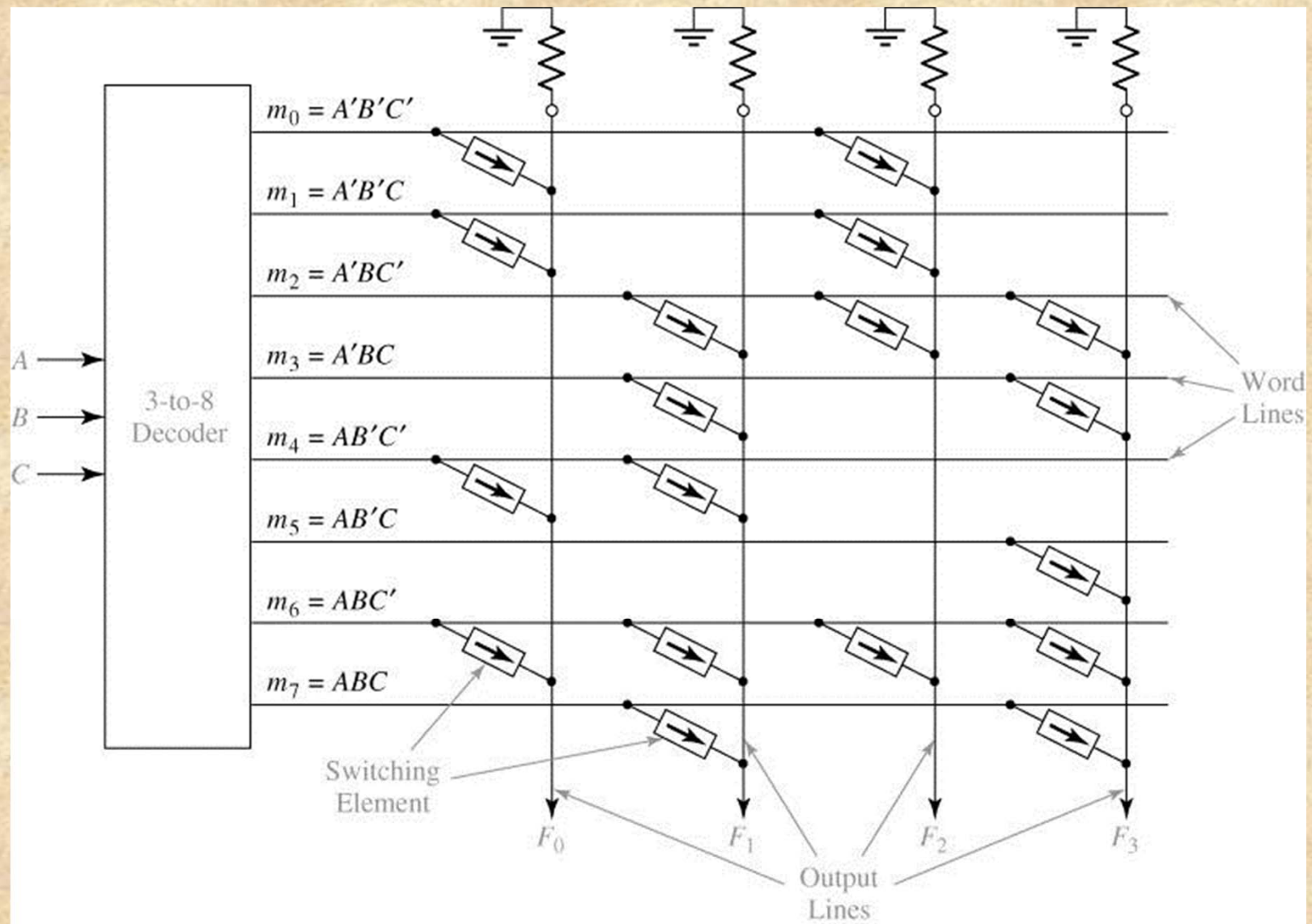
- Another way to realize is to use a 3-to-8 decoder



Read-Only Memories (5/6)

- Example 2:
 - Convert hexadecimal digits into 7-bit ASCII codes.
 1. Decide the inputs and outputs
 2. Develop a truth table
 3. Realize the circuit
 1. Minterm expansion → simplification → circuit
 2. Minterm expansion → decoder → circuit

Read-Only Memories (6/6)

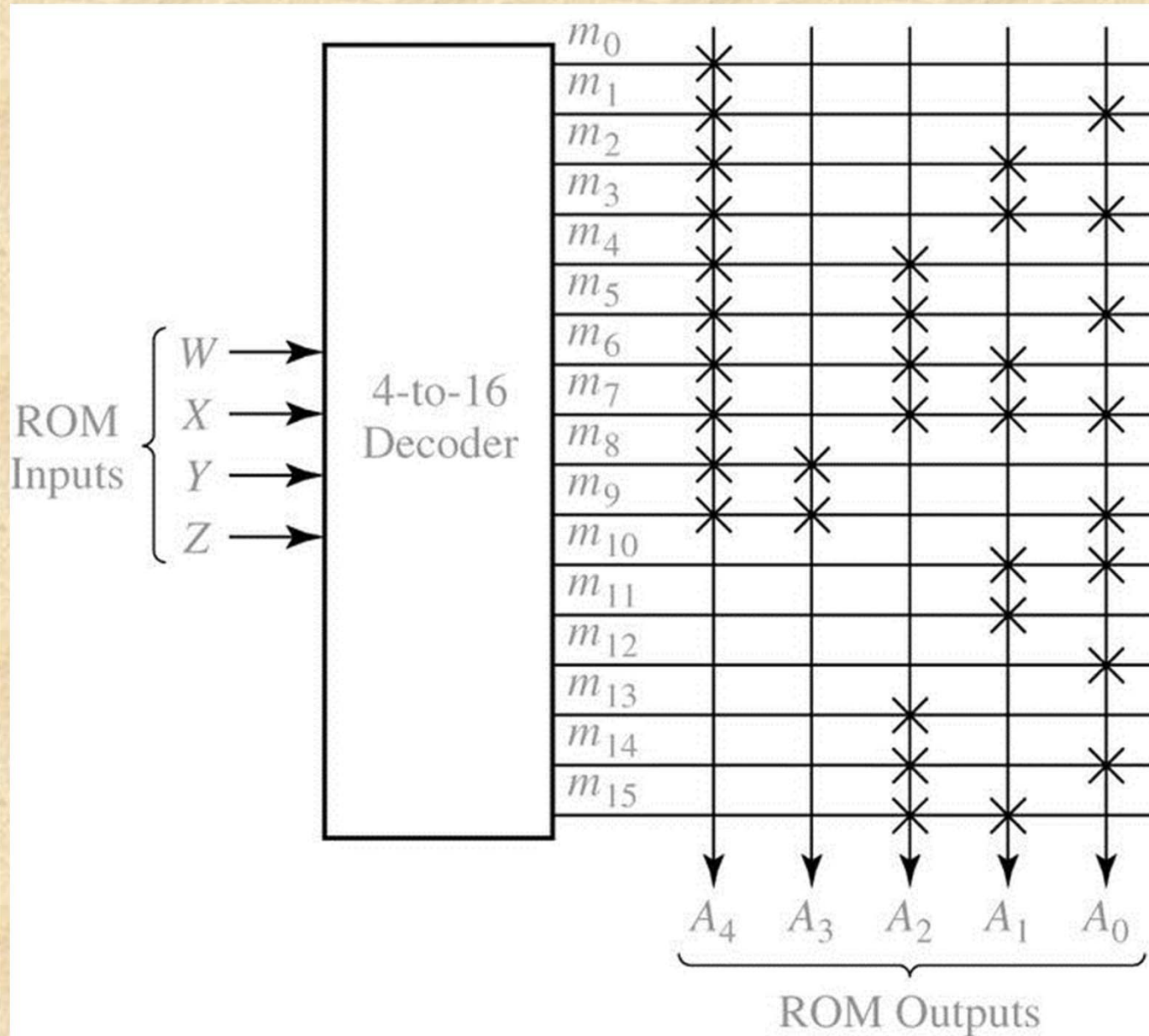

An X indicates that the switching element is present and connected, and no X indicates that the corresponding element is absent or not connected.

Programmable Logic Devices (1/12)


- ROMs use decoders and switching elements to OR minterms.
- But it is only a good choice when the number of inputs is small. Why?
- If we have many inputs, the required decoder will have to be very large.

Programmable Logic Devices (2/12)

- Programmable Logic Devices (PLD) can be used when the number of inputs is large.
 - Programmable Logic Arrays (PLA)
 - Programmable Array Logics (PAL)

Programmable Logic Devices (3/12)

- Programmable logic arrays (PLA)

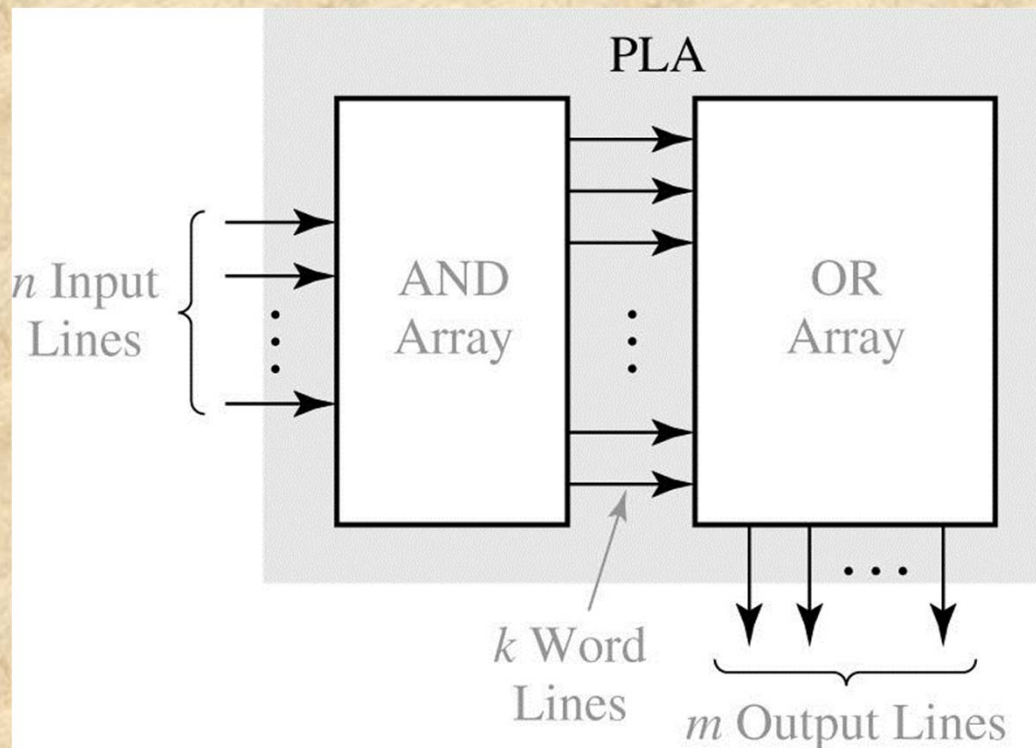


k does not have to be 2^n

Programmable Logic Devices (3/12)


- Example 1:
 - $F_0 = A'B' + AC'$
 - $F_1 = AC' + B$
 - $F_2 = A'B' + BC'$
 - $F_3 = B + AC$

Programmable Logic Devices (4/12)

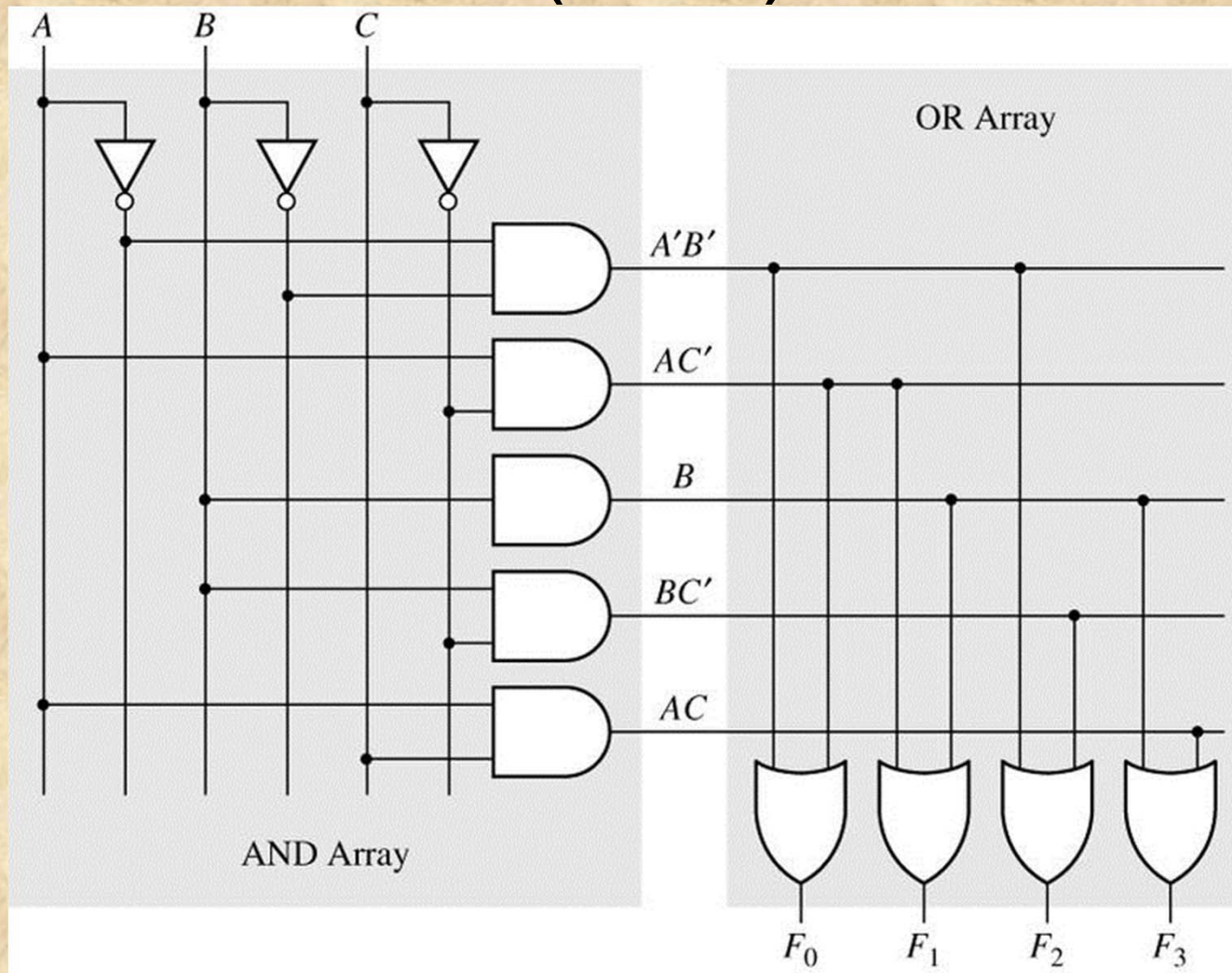

Programmable Logic Devices (5/12)

The implementation using PLA

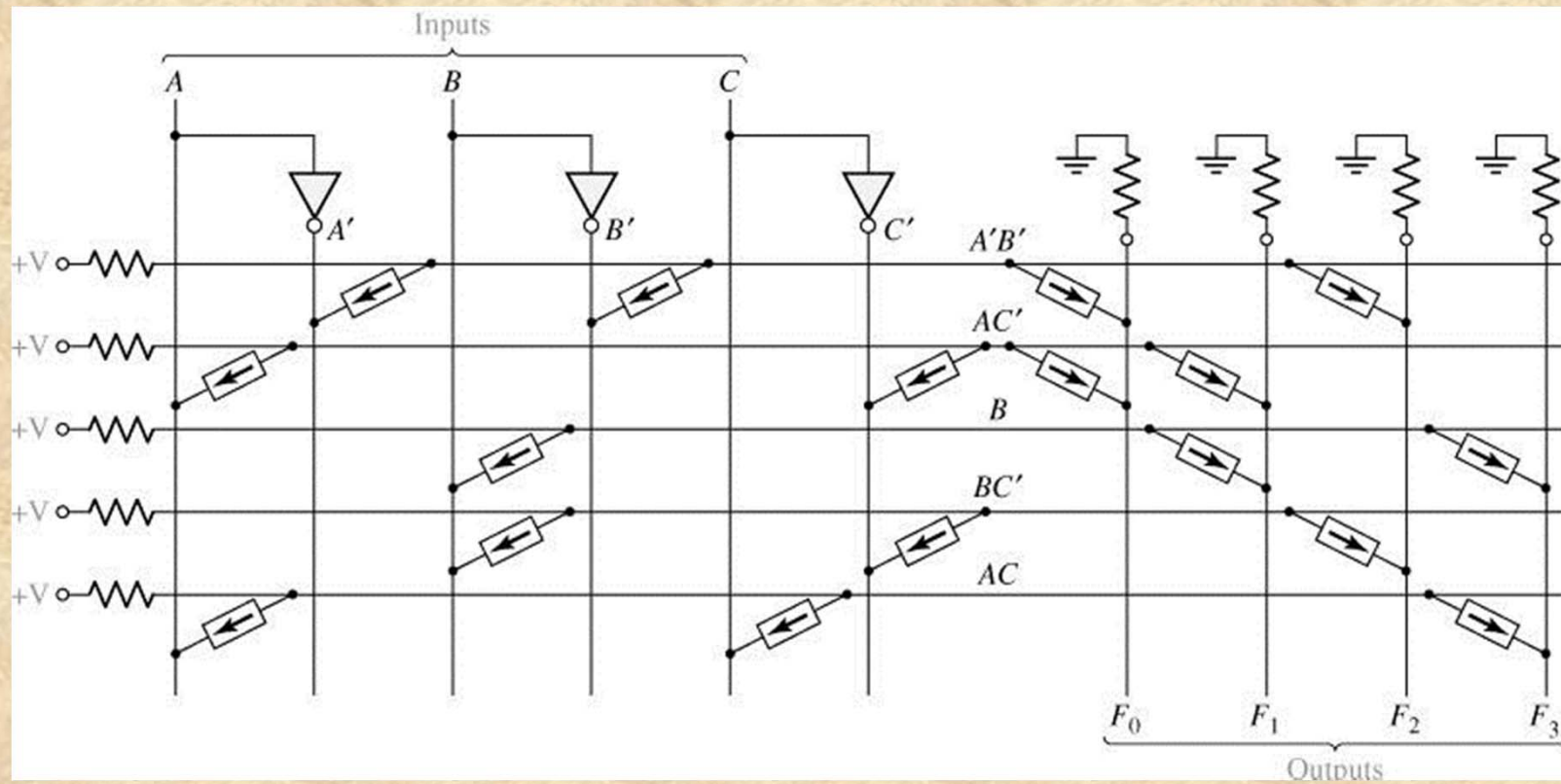

Programmable Logic Devices (6/12)


- Example 2:
 - $f_1 = a'bd + abd + ab'c' + b'c$
 - $f_2 = c + a'bd$
 - $f_3 = bc + ab'c' + abd$

Programmable Logic Devices (7/12)

- Truth table used by PLA
- Note: the number of rows is not 2^n , where n is the number of inputs.

a	b	c	d	f_1	f_2	f_3
0	1	-	1	1	1	0
1	1	-	1	1	0	1
1	0	0	-	1	0	1
-	0	1	-	1	0	0
-	-	1	-	0	1	0
-	1	1	-	0	0	1

Programmable Logic Devices (7/12) (cont)

 

(b) PLA structure

Programmable Logic Devices (8/12)


- Programmable Logic Devices (PLD) can be used when the number of inputs is large.
 - Programmable Logic Arrays (PLA)
 - Programmable Array Logics (PAL)

Programmable Logic Devices (9/12)

- PALs are similar to PLAs, but the OR array is fixed and the AND array is programmable.

Programmable Logic Devices (10/12)

 - Example 3:
 - $F = I_1 I_2' + I_1' I_2$



Programmable Logic Devices (11/12)

- Example 4:

- $\text{Sum} = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$

- $C_{out} = XC_{in} + YC_{in} + XY$

- If the PAL has two OR gates both of which have four inputs, one of the inputs for C_{out} has the input of 0, why?

Programmable Logic Devices (12/12)

